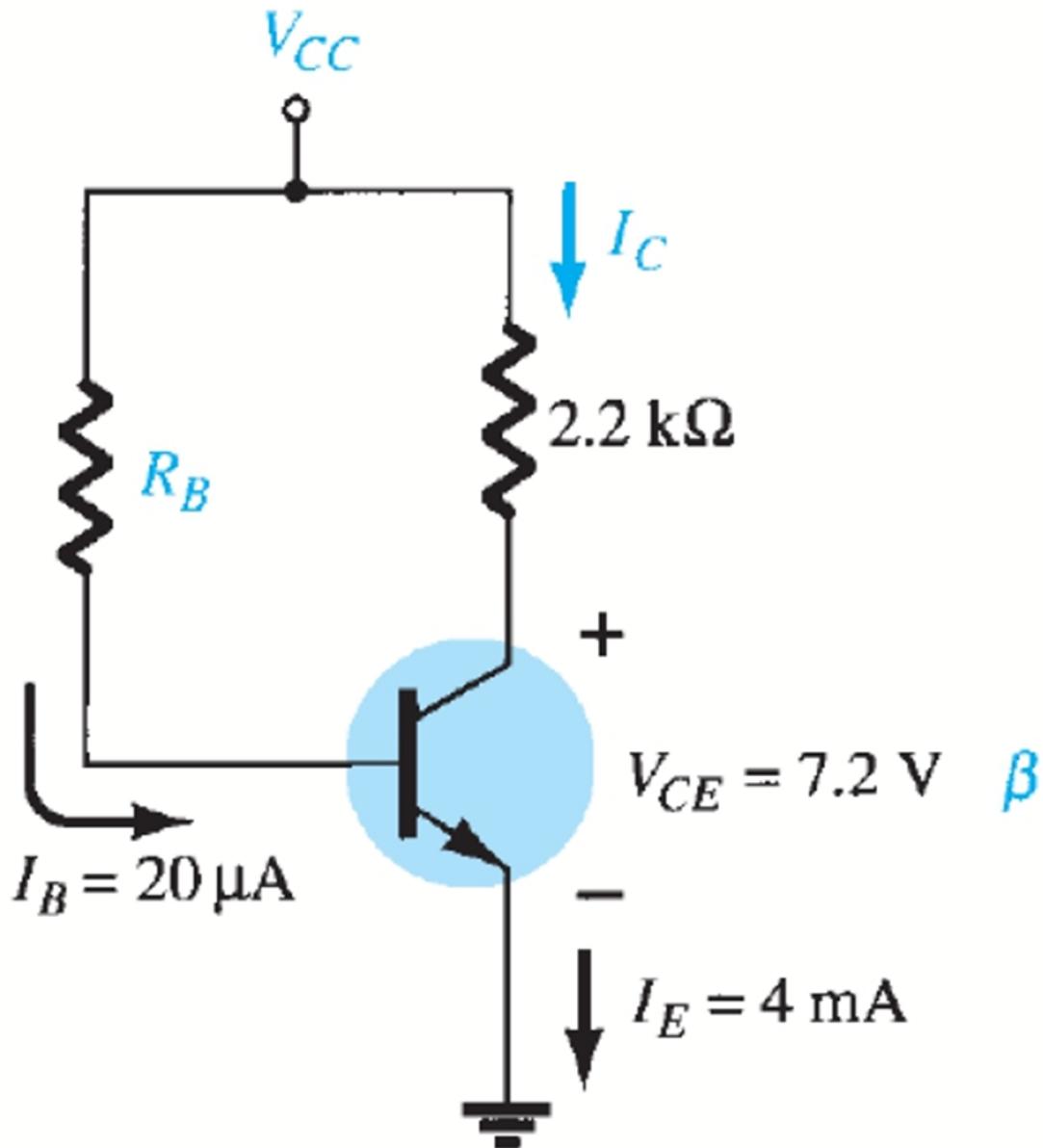


1. Given the information appearing in figure 1 (a), determine:
a) I_C , b) V_{CC} , c) β , d) R_B



$$I_E = (\beta + 1)I_B \Rightarrow \beta = \frac{4 \text{ mA}}{20 \mu\text{A}} - 1 = 199$$

$$I_C = \beta \cdot I_B = 199 \cdot 20 \mu\text{A} = 3.98 \text{ mA}$$

KVL for output loop:

$$V_{CC} - I_C \cdot 2.2 \text{ k}\Omega - V_{CE} = 0 \Rightarrow V_{CC} = 3.98 \text{ mA} \cdot 2.2 \text{ k}\Omega + 7.2 \text{ V}$$


$$V_{CC} = 15.96 \text{ V}$$

KVL for input loop:

$$V_{CC} - I_B R_B - V_{BE} = 0 \Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{(15.96 - 0.7)}{20 \mu\text{A}}$$

$$R_B = 765 \text{ k}\Omega$$

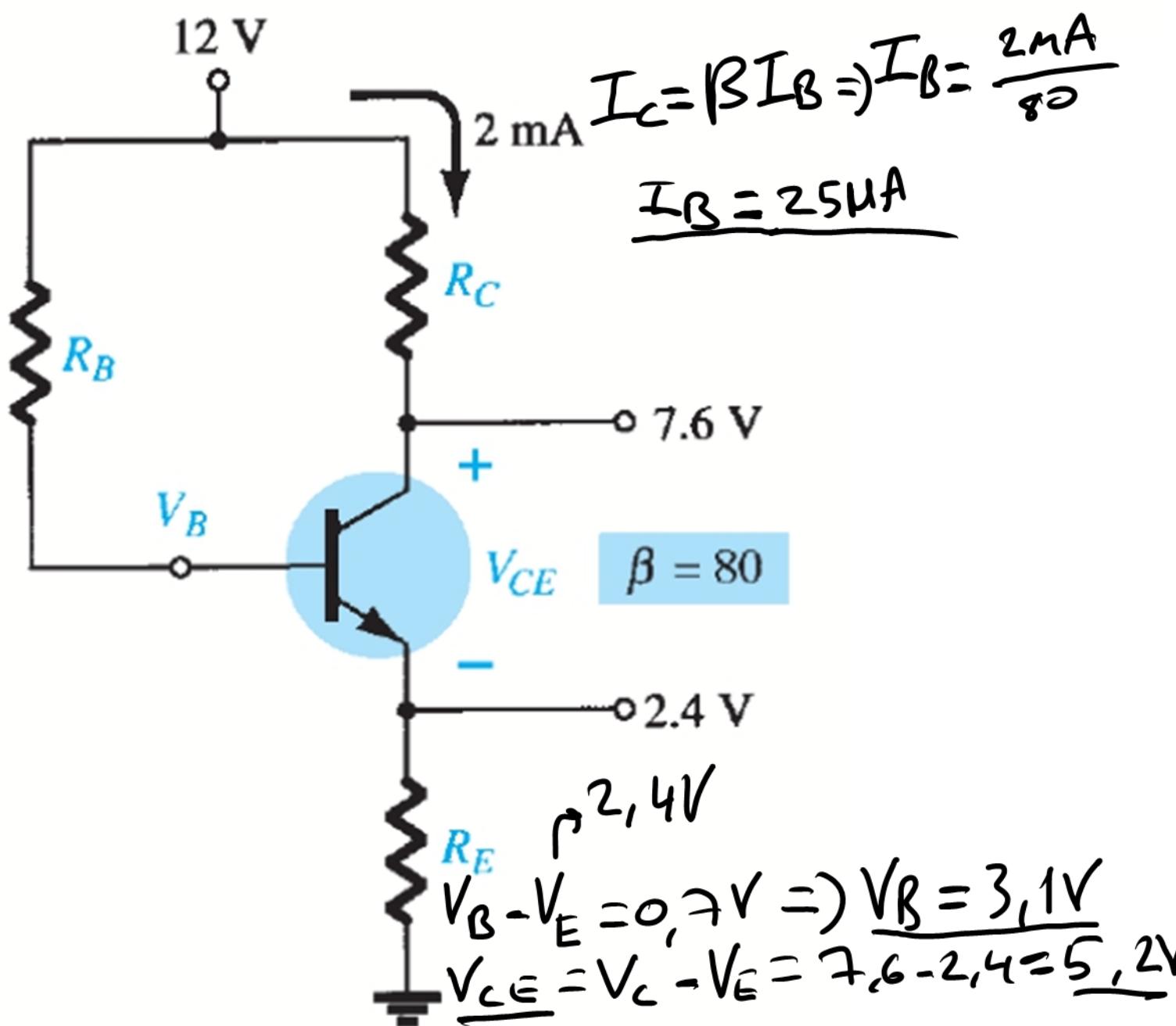2. Given the information provided in figure 1 (b), determine:
 a) R_C , b) R_E , c) R_B , d) V_{CE} , e) V_B



KVL for input:

$$12 - i_B R_B - V_B = 0 \Rightarrow R_B = \frac{12\text{V} - V_B}{i_B} = \frac{12\text{V} - 3,1\text{V}}{25\mu\text{A}} = 356\text{k}\Omega$$


KVL for output:

$$12 - i_C R_C - V_C = 0 \Rightarrow R_C = \frac{12 - V_C}{i_C} = \frac{(12 - 7,6)\text{V}}{2\text{mA}} = 2,2\text{k}\Omega$$

$$I_E = (\beta + 1) I_B = 2\text{mA}$$

$$R_E = \frac{V_E}{I_E} = \frac{2,4\text{V}}{2\text{mA}} = 1,2\text{k}\Omega$$

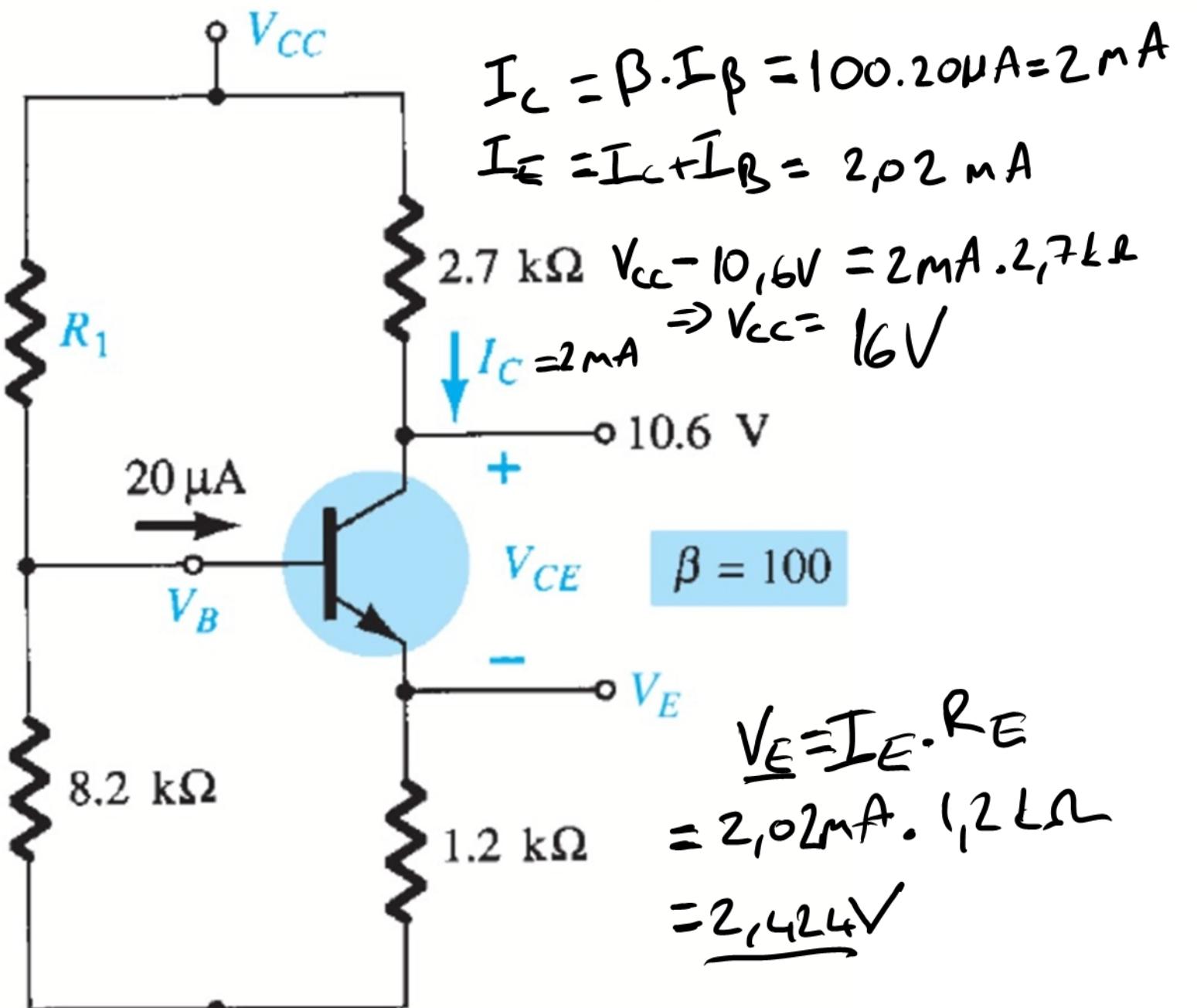3. Given the information appearing in figure 2 (a), determine:
 a) I_C , b) V_E , c) V_{CC} , d) V_{CE} , e) V_B , f) R_1



$$V_{BE} = 0,7 \text{ V} = V_B - 2,424 \quad \underline{\underline{V_{CE} = 10,6 - 2,424}} \\ \underline{\underline{- 8,176 \text{ V}}} \\ \Rightarrow V_B = 3,124 \text{ V}$$


$$V_{R1} = 16 - 3,124 = 12,876$$

$$I_{R1} = 20 \mu A + \frac{3,124 \text{ V}}{8,2 \text{ k}\Omega} = 401 \mu A$$

$$\underline{\underline{R_1 = \frac{12,876 \text{ V}}{401 \mu A} = 32,11 \text{ k}\Omega}}$$

4. For the collector-feedback configuration of figure 2 (b), determine:

- a) I_B , b) I_C , c) V_C

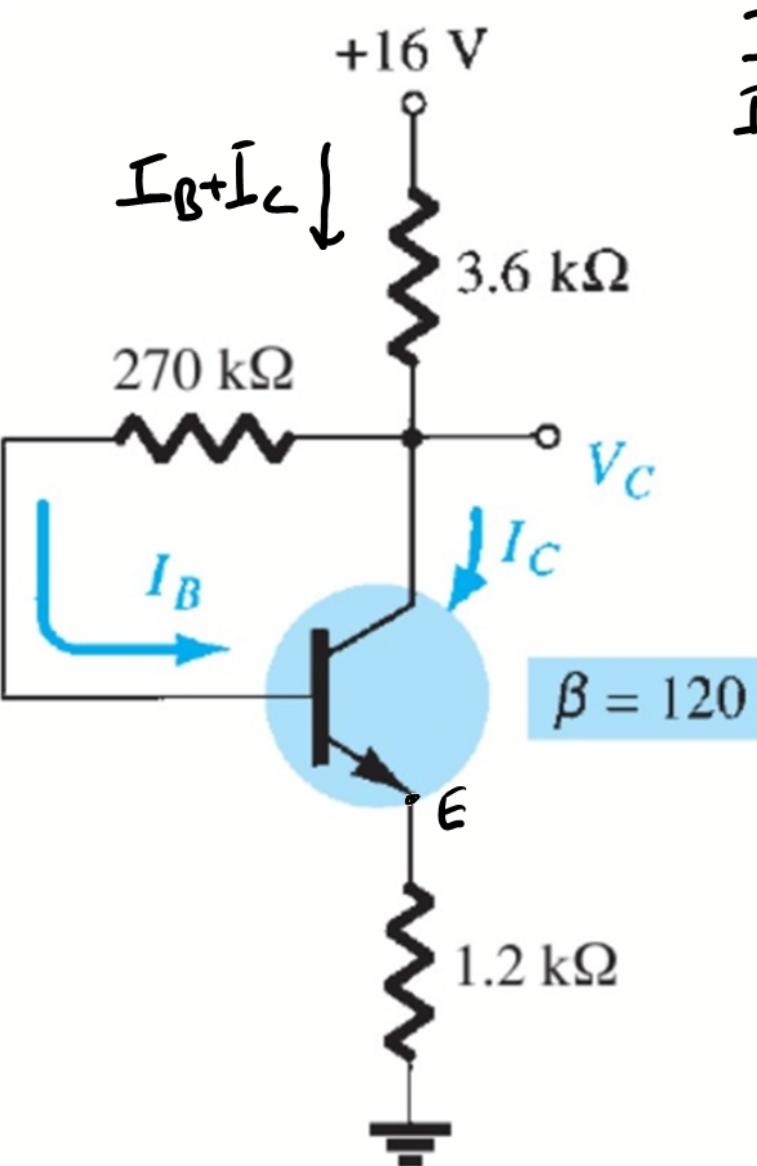

$$I_c = \beta \cdot I_B = 120 I_B$$

$$I_E = (\beta + 1) \cdot I_B = 121 I_B$$

$$16V - 121I_B \cdot 3,6k\Omega - I_B \cdot 270k\Omega - 0,7V - 121I_B \cdot 1,2k\Omega = 0$$

$$\Rightarrow I_B = \frac{15,3V}{850,8k} = 17,98 \text{ mA}$$


$$I_c = \beta I_B = 120 \cdot 17,98 \text{ mA} = 2,158 \text{ mA}$$

$$16V - V_C = (I_B + I_C) \cdot 3,6k\Omega \Rightarrow V_C = 16V - 2,176 \text{ mA} \cdot 3,6k\Omega$$

$$\Rightarrow V_C = 8,17$$

5. For the voltage feedback network of figure 3 (a), determine:

- a) I_C , b) V_C , c) V_E , d) V_{CE}

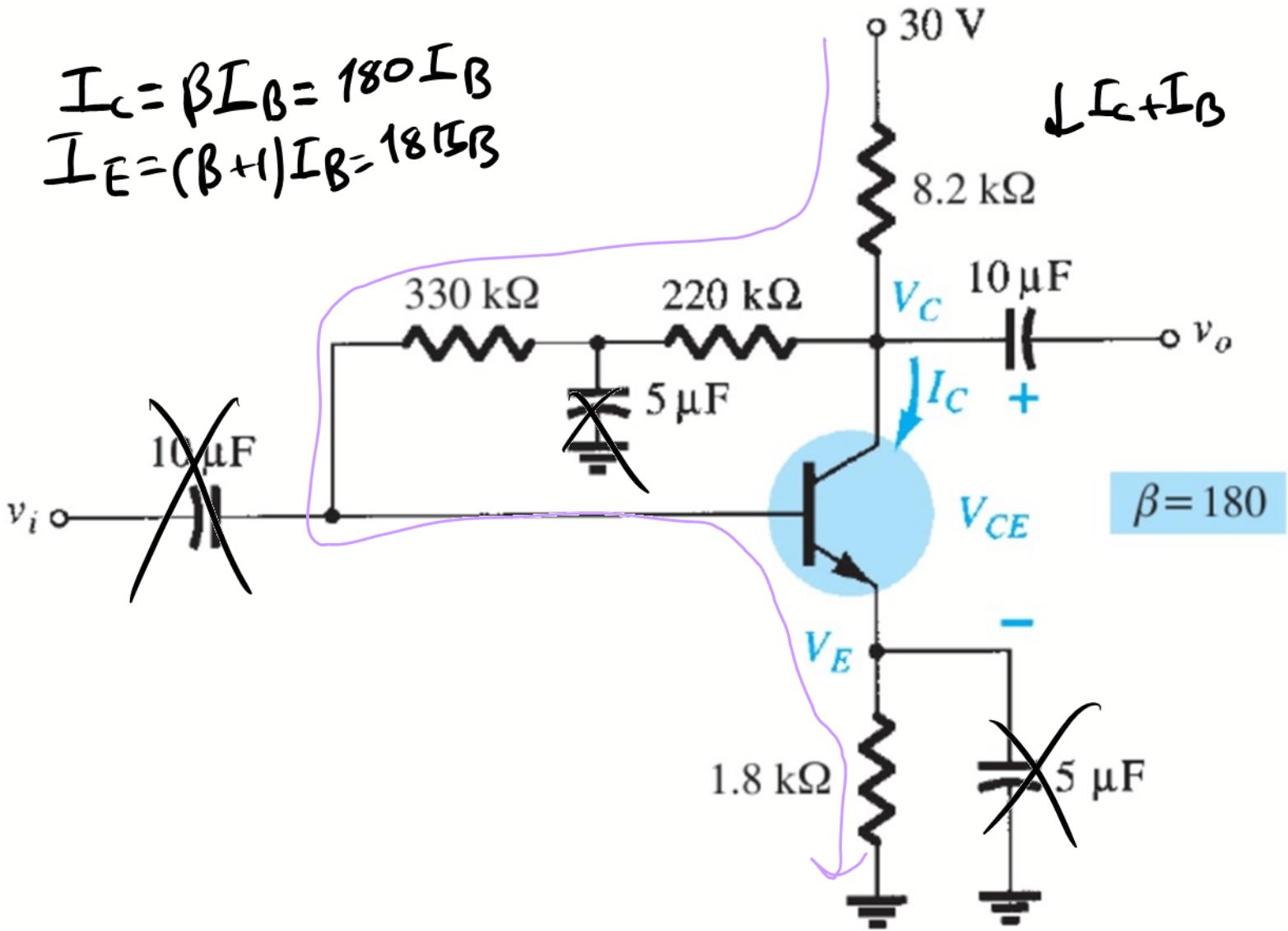

$$30V - (181I_B) \cdot 8.2k\Omega - 550k\Omega \cdot I_B - 0.7V - 181I_B \cdot 1.8k\Omega = 0$$

$$\Rightarrow I_B = \frac{(30 - 0.7)V}{2360k\Omega} = 12.42mA$$

$$I_E = 181I_B = 2.248mA$$

$$\underline{I_C = 180I_B = 2.1236mA}$$


$$30V - V_C = I_C \cdot 8.2k\Omega \Rightarrow \underline{V_C = 11.66V}$$

$$\underline{V_E = I_E \cdot 1.8k\Omega = 4.05V}$$

$$\underline{V_{CE} = (11.66 - 4.05)V = 7.61V}$$

6. For the network of 3 (b), determine:

- a) I_E , b) V_C , c) V_{CE}

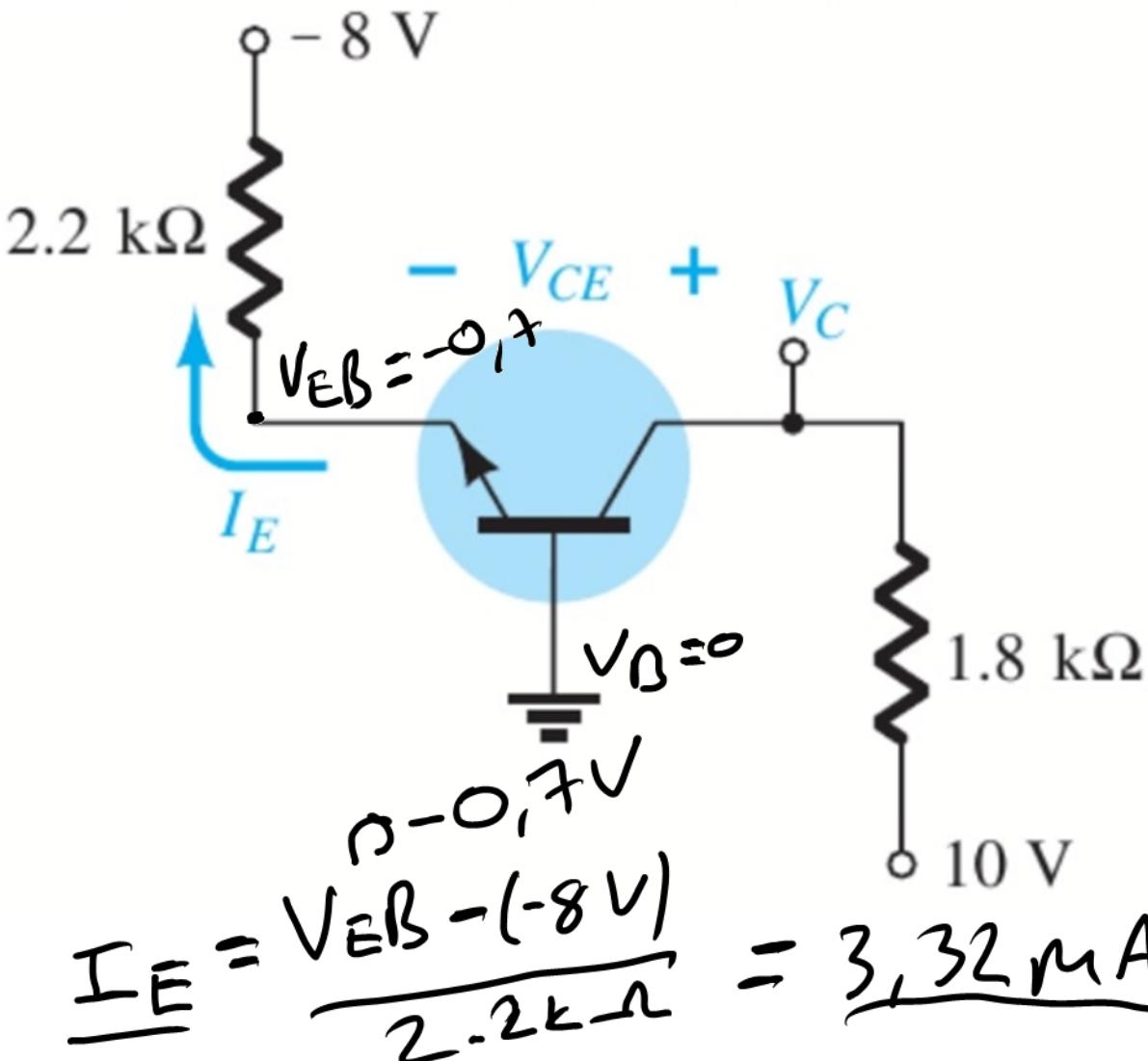

$I_C \approx I_E = 3.32mA$ (we don't know β
so I used approxim
value)

$$10 - V_C = 1.8k\Omega \cdot 3.32mA \Rightarrow \underline{\underline{V_C = 4.024V}}$$

$$\underline{\underline{V_{CE} = 4.024V - (-0.7V) = 4.724V}}$$