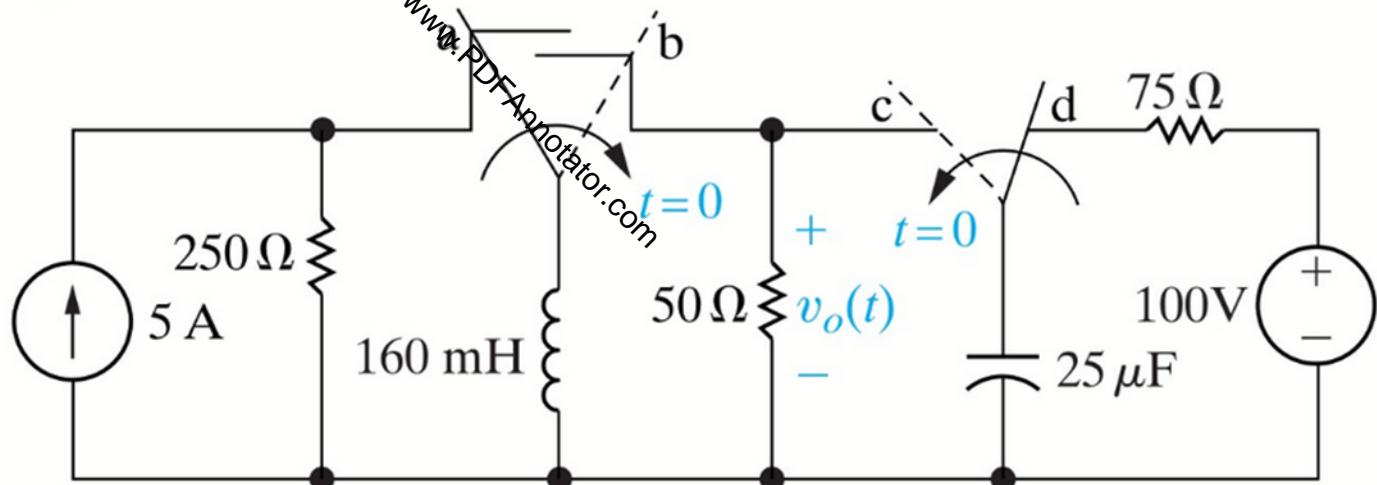



- 8.11** The two switches in the circuit seen in Fig. P8.11 operate synchronously. When switch 1 is in position a, switch 2 is in position d. When switch 1 moves to position b, switch 2 moves to position c. Switch 1 has been in position a for a long time. At $t = 0$, the switches move to their alternate positions. Find $v_o(t)$ for $t \geq 0$.

Figure P8.11



$$i_L(0^-) = 5A$$

$$V_C(0^-) = 100V$$

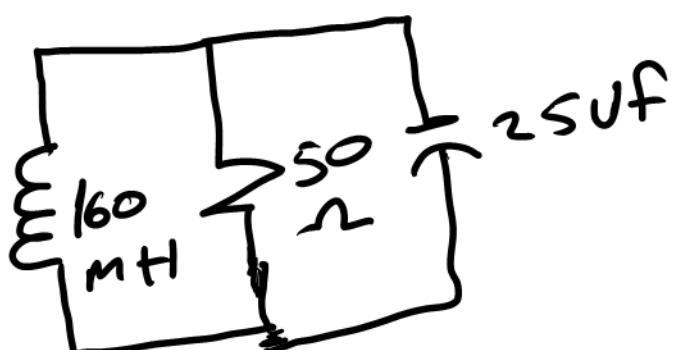

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{160 \cdot 10^{-3} \cdot 25 \cdot 10^{-6}}} = 500 \text{ rad/s}$$

$$\alpha = \frac{1}{RC} = \frac{1}{2.50 \cdot 25 \cdot 10^{-6}} = 400 \text{ rad/s}$$

$\omega_0^2 > \alpha^2 \rightarrow$ under damped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 300 \text{ rad/s}$$

$$\beta_1 = V_0 = 100 \text{ V}$$

$$i_C(0) = -i_L(0) - i_R(0) = -5 - \frac{100}{50} = -7$$

$$-\alpha\beta_1 + \omega_d\beta_2 = \frac{1}{C} \cdot i_C(0)$$

$$-400 \cdot 100 + 300 \cdot \beta_2 = \frac{1}{25 \cdot 10^{-6}} \cdot -7 \Rightarrow \beta_2 = -800$$


$$V_o(t) = e^{-\alpha t} \cdot [\beta_1 \cdot \cos(\omega_d t) + \beta_2 \cdot \sin(\omega_d t)]$$

Insert everything

$$V_o(t) = e^{-400t} \cdot [100 \cos(300t) - 800 \sin(300t)] \sqrt{}$$

- 8.27** Assume that at the instant the 2 A dc current source is applied to the circuit in Fig. P8.27, the initial current in the 25 mH inductor is 1 A, and the initial voltage on the capacitor is 50 V (positive at the upper terminal). Find the expression for $i_L(t)$ for $t \geq 0$ if R equals 12.5 Ω .

Figure P8.27

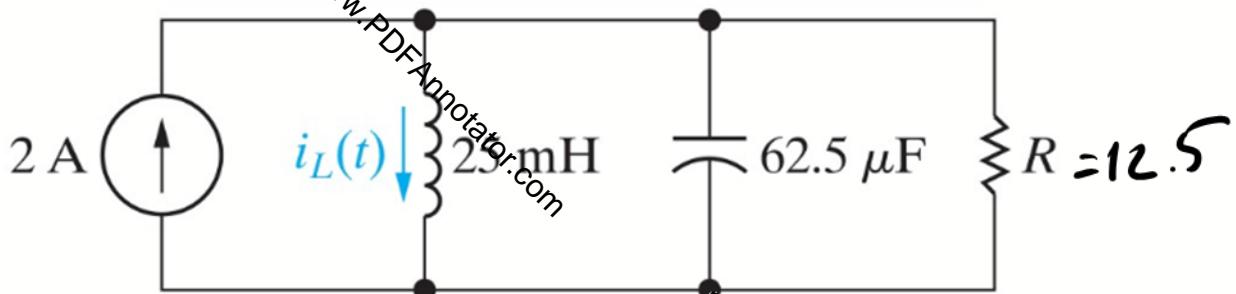

$$i_L(0^-) = 1 \text{ A} \quad V_c(0^-) = 50 \text{ V}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{25 \cdot 10^{-3} \cdot 62.5 \cdot 10^{-6}}} = 800 \text{ rad/s}$$

$$\Rightarrow \alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 12.5 \cdot 62.5 \cdot 10^{-6}} = 640 \text{ rad/s}$$

$\omega^2 > \alpha^2$ Underdamped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 480 \text{ rad/s}$$

$$i_L(t) = e^{-\alpha t} \cdot [\beta'_1 \cos(\omega_d t) + \beta'_2 \sin(\omega_d t)] + I_f$$

$$= \beta'_1 + I_f \Rightarrow 1 = \beta'_1 + 2 \Rightarrow \beta'_1 = -1$$

$$\frac{V(0)}{L} = -\beta'_1 \alpha + \beta'_2 \omega_d \rightarrow \frac{50}{25 \cdot 10^{-3}} = 640 + 480 \beta'_2$$

$$\Rightarrow \beta'_2 = 2.833$$


$$i_L(t) = e^{-640t} \cdot [-1 \cos(480t) + 2.833(480t)] + 2 \text{ A}$$

8.35 The switch in the circuit in Fig. P8.35 has been in the left position for a long time before moving to the right position at $t = 0$. Find

a) $i_L(t)$ for $t \geq 0$,

b) $v_C(t)$ for $t \geq 0$.

Figure P8.35

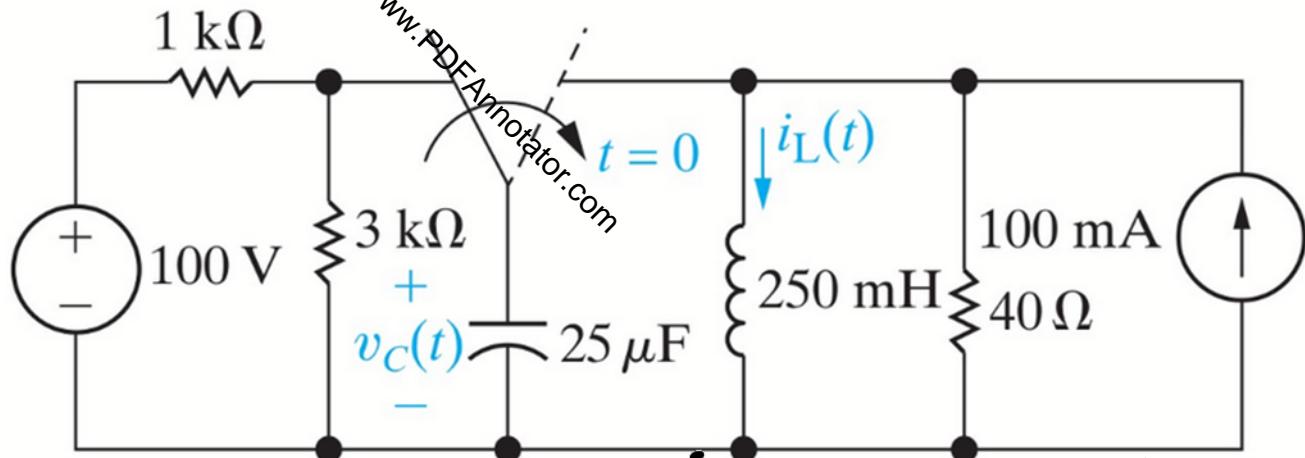

$$V_0 = \frac{3}{4} \cdot 100 = 75$$

$$i_0 = 100 \text{ mA} = 0.1 \text{ A}$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{250 \times 10^{-3} \times 25 \times 10^{-6}}} = 400 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 40 \cdot 25 \cdot 10^{-6}} = 500 \text{ rad/s}$$

$\alpha^2 > \omega_0^2$ Overdamped

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -500 \pm \sqrt{500^2 - 400^2}$$

$$s_1 = -200, s_2 = -800$$

$$s_1 = -200, s_2 = -800$$

1st eq. for $t=0$

$$A'_1 + A'_2 + 0.1 = 0.1$$

$$A'_1 + A'_2 = 0 / \times 50 + -50A'_1 - 200A'_2 = 75 \Rightarrow A'_1 = \frac{1}{2}$$

$$\frac{2nd eq. for t=0}{250 \times 10^{-3}(-200A'_1 - 800A'_2)} = 75$$

$$A'_2 = -\frac{1}{2}$$

Produced with a Trial Version of PDF Annotator www.PDFAnnotator.com

$$i_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + I_f \quad (\text{insert everything})$$

$$i_c(t) = \frac{e^{-200t} - e^{-800t}}{2} + 0,1 \text{ A} \quad (a)$$


$$V_c(t) = L \left(s_1 A_1 e^{s_1 t} + s_2 A_2 e^{s_2 t} \right) \quad (\text{insert everything})$$

$$V_c(t) = 250 \times 10^{-3} \cdot (-200.0.5 \cdot e^{-200t} - 800.0.5 \cdot e^{-800t})$$

$$= 0,25 \cdot (-100e^{-200t} - 400e^{-800t}) = -25e^{-200t} - 100e^{-800t} \text{ V} \quad (b)$$

- 8.47** The switch in the circuit shown in Fig. P8.47 has been closed for a long time. The switch opens at $t = 0$. Find $v_o(t)$ for $t \geq 0^+$.

Figure P8.47

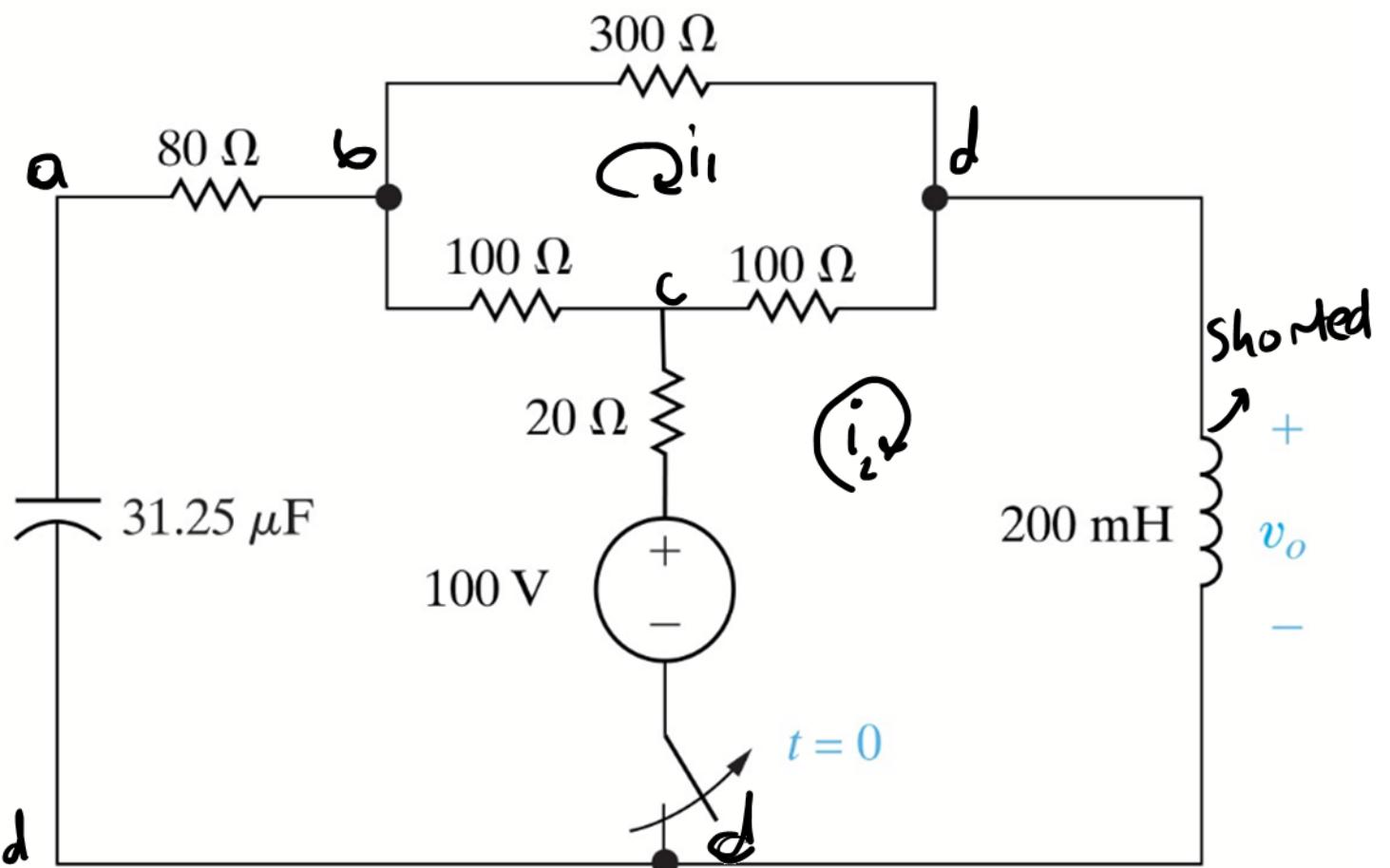

$$\begin{aligned} 300i_1 + 100(i_1 - i_2) + 100i_1 &= 0 \quad i_1 = 0,2 \text{ A} \\ -100V + 20i_2 + 100(i_2 - i_1) &= 0 \quad i_2 = 1 \text{ A} \end{aligned}$$

$$= V_C(0) = V_{ad} = V_{cd} = -100 + 20 \cdot 1 + 100 \cdot 0,2 = \underline{-60 \text{ V}}$$

$$R_{eq}(t>0) = \left(\frac{300}{200} \parallel \left(\frac{100}{100+100} \right) \right) + 80 = 200 \Omega$$



$$\omega = \frac{200}{200} = 500 \text{ rad/s}$$

$$\omega_0 = \sqrt{0,2 \times 31,25 \times 10^{-6}} = 400 \text{ rad/s}$$

$\omega^2 > \omega_0^2$ overdamped

$$s_1, s_2 = -500 \pm \sqrt{500^2 - 400^2} \Rightarrow s_1 = -200, s_2 = -800$$

$$i_0 = i_2 = 1 = A_1 + A_2 \quad ①$$

$$\text{L. } \frac{d i_C(0)}{dt} = V_C(0) = -60 = (A_1 \cdot -200 + A_2 \cdot -800) \cdot 0,2$$

$$3 = -2A_1 - 8A_2 \quad ② \quad 2 \cdot (① + ②) \Rightarrow A_1 = \frac{1}{6}, A_2 = \frac{5}{6}$$


$$V_o(t) = \text{L. } \frac{d i_C(0)}{dt} = (A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}) \cdot L$$

$$= \left(\frac{-200 \cdot e^{-200t} - 5 \cdot 800 \cdot e^{-800t}}{6} \right) \cdot 0,2$$


$$= 6,67 \cdot e^{-200t} - 133 \cdot e^{-800t} \text{ V}$$

- 8.54** The two switches in the circuit seen in Fig. P8.55 operate synchronously. When switch 1 is in position a, switch 2 is closed. When switch 1 is in position b, switch 2 is open. Switch 1 has been in position a for a long time. At $t = 0$, it moves instantaneously to position b. Find $v_c(t)$ for $t \geq 0$.

Figure P8.54

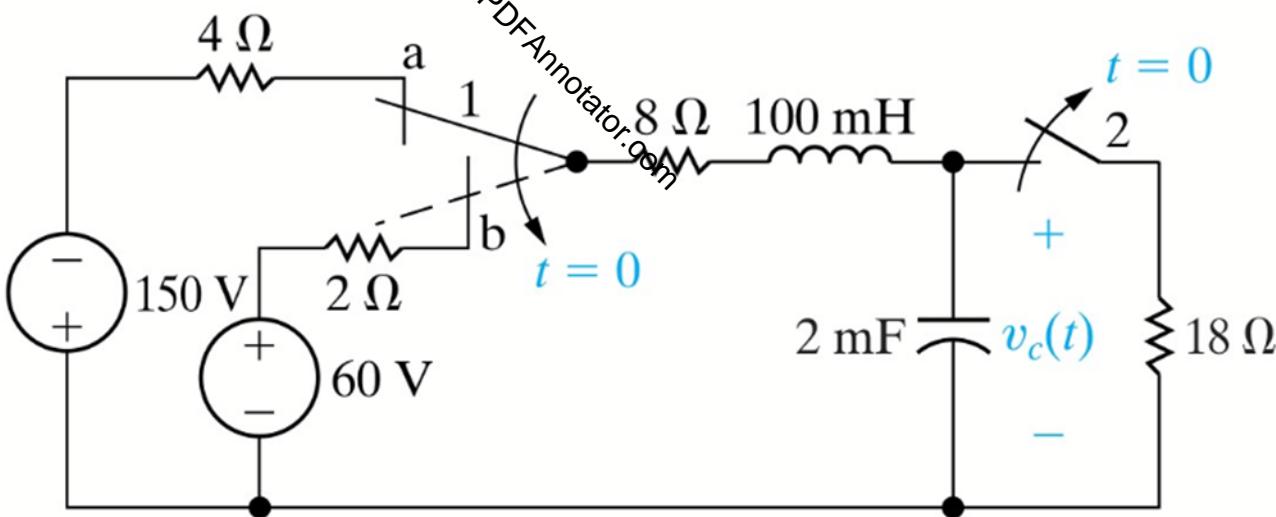


initial:

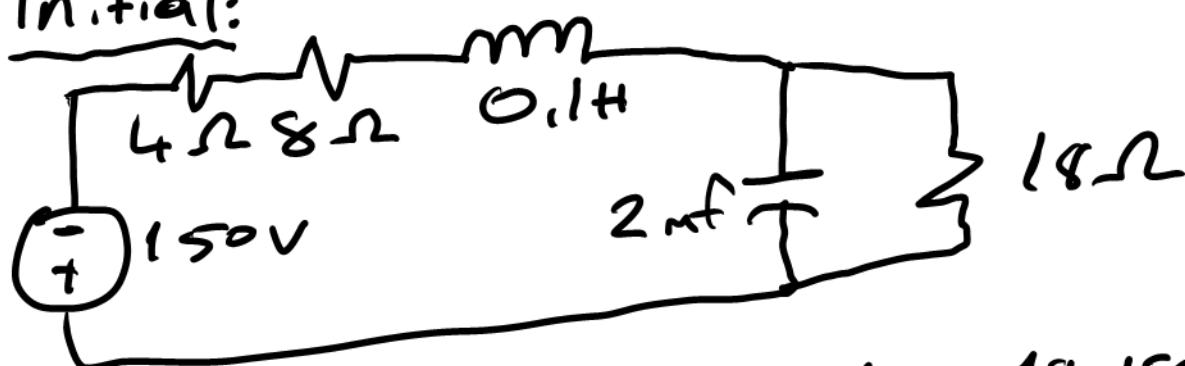

$$-150 = 30 \cdot i_L(0) \Rightarrow i_L(0) = -5A \quad V_C(0) = \frac{18}{30} \cdot -150 = 90V$$

$t > 0$:

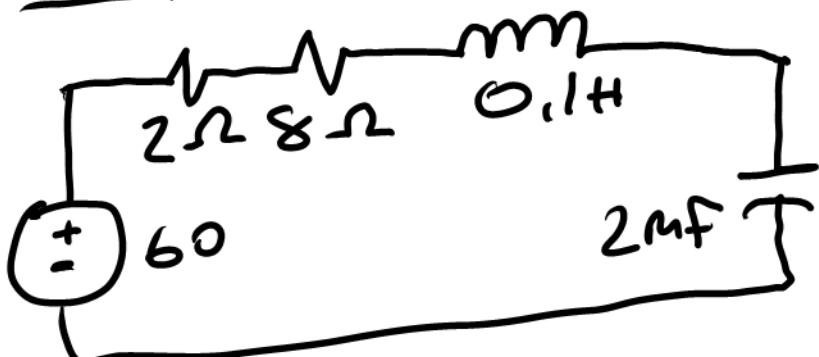

$$R_{eq} = 10\Omega$$

$$w_0 = \sqrt{\frac{1}{0.1 \times 2 \times 10^{-3}}} = 70.71 \text{ rad/s}$$

Produced with a trial version of PDF Annotator

$$\omega = \frac{10}{2.0.1} = 50 \text{ rad/s}$$

$w_0^2 > \omega^2$ under damped

$$w_d = \sqrt{70.71^2 - 50^2} = 50 \text{ rad/s}$$

$$V_C(0) = B'_1 + V_f = -90 = B'_1 + 60 \Rightarrow B'_1 = -150$$


$$\frac{i(0)}{C} = -B'_1 \cdot \omega + B'_2 \cdot w_d \Rightarrow \frac{-5}{2 \times 10^{-3}} = 150.50 + B'_2 \cdot 50$$

$$\Rightarrow B'_2 = -200$$

$$V_C(t) = e^{-50t} \cdot [-150 \cos(50t) - 200 \sin(50t) + 60] \text{ V}$$

- 9.32 Find \mathbf{I}_b and Z in the circuit shown in Fig. P9.32 if $\mathbf{V}_g = 25 \angle 0^\circ \text{ V}$ and $\mathbf{I}_a = 5 \angle 90^\circ \text{ A}$.

Figure P9.32

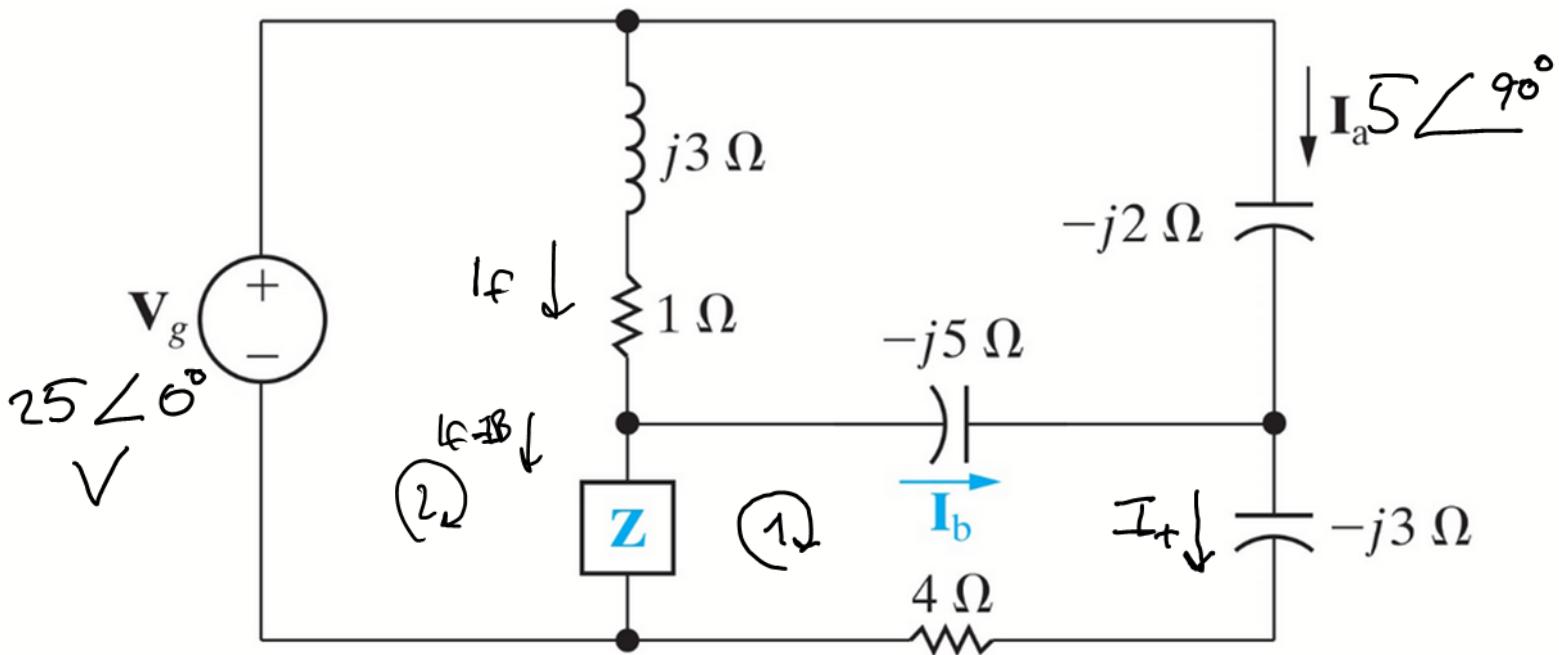

$$V_{-j2} = 5 \angle 90^\circ \cdot -j2 \Omega = 5 \cos(90) + 5 \sin(90)j \cdot -j2 \Omega$$

$$= 5 \cdot -j2 = -10j^2 = \underline{10V}$$

KVL AT OUTER LOOP:

$$-25 + 10 + (4+j3) \cdot I_r = 0 \Rightarrow I_r = \frac{15}{4+j3} \cdot \frac{4+j3}{4+j3} = 2,4 + 1,8j$$

$$I_b = I_r - I_a = 2,4 + 1,8j - 5j = \underline{2,4 - 3,2j A}$$

KVL AT Loop 1:

$$-V_2 + I_b \cdot (-j5) + I_r \cdot (-j3 + 4) = 0$$

$$\Rightarrow V_2 = (2,4 - 3,2j) \cdot (-j5) + (2,4 + 1,8j) \cdot (-j3 + 4)$$

$$= \underline{-12j - 16} \quad \underline{15}$$

$$\Rightarrow V_2 = -12j - 1$$

KVL AT Loop 2:

$$-25 + (1+j3) I_f + (-12j - 1) = 0$$

$$I_f = \frac{12j + 26}{3j+1} \cdot \frac{3j-1}{3j-1} = \frac{-36 - 12j + 78j - 26}{-9 - 1} = \frac{62 - 62}{-10}$$

$$= 6,6j - 6,2 A$$


$$I_2 = I_f - I_b = -3,4j + 3,8A$$

$$E = \frac{-12j - 1}{-3,4j + 3,8} \cdot \frac{-3,4j - 3,8}{-3,4j - 3,8} = 1,42 - 1,88j \Omega$$


Produced with a Trial Version of PDF Annotator - www.PDFAnnotator.com

9.45 Use source transformations to find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.45.

Figure P9.45

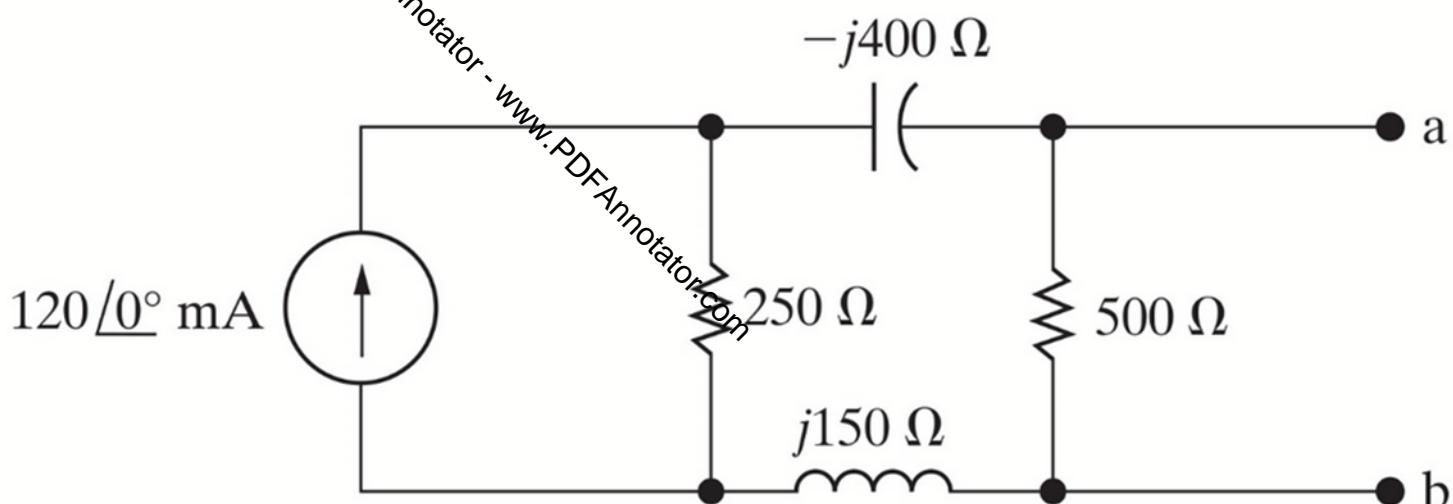
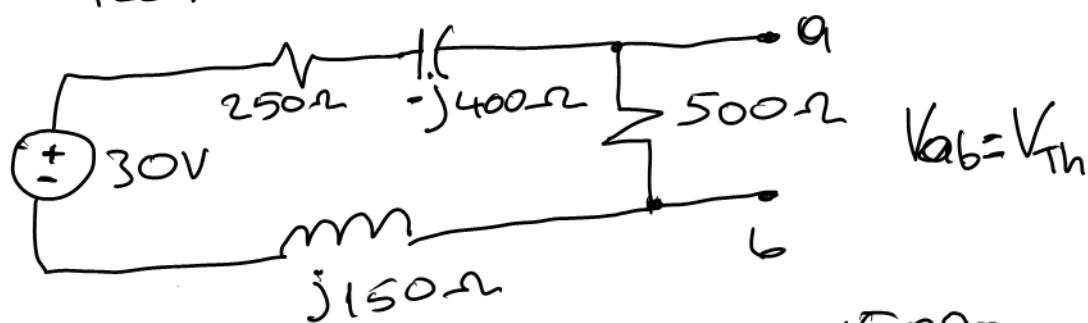
$$V = 120 \text{ mA} \cdot 250 \Omega = 30 \text{ V}$$



$$V_{Th} = 30 \cdot \frac{500}{500 + 250 + j150 - j400} = \frac{15000}{750 - 250j} = \frac{60}{3 - j} \cdot \frac{-3 - j}{-3 - j} = \frac{-180 - 60j}{-10} = 18 + 6j \text{ V}$$


$$Z_{Th} = \frac{(250 - j250) \cdot 500}{750 - j250} = \frac{500 - 500j}{3 - j} \cdot \frac{-3 - j}{-3 - j} = \frac{-1000 - 2000j}{-10} = \frac{-1000 + 2000}{-10} \Omega$$

$$= -100j + 200 \Omega$$



P9.46 Find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.46.

Figure P9.46

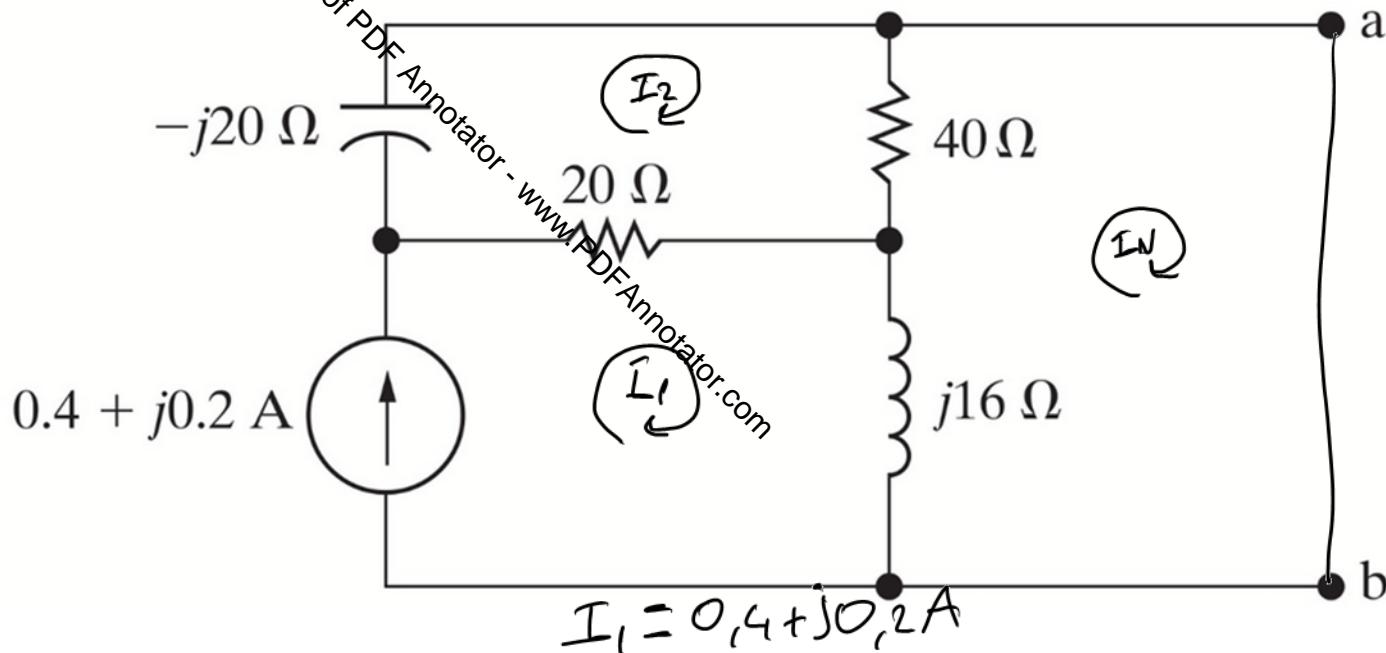


$$I_2(-20j) + (I_2 - I_N) \cdot 40 + (I_2 - 0.4 - 0.2j) \cdot 20 = 0$$

$$I_2(60 - 20j) - 40I_N - 8 - 4j = 0 \quad (1)$$

$$(I_N - 0.4 - 0.2j) \cdot 16j + (I_N - I_2) \cdot 40 = 0$$
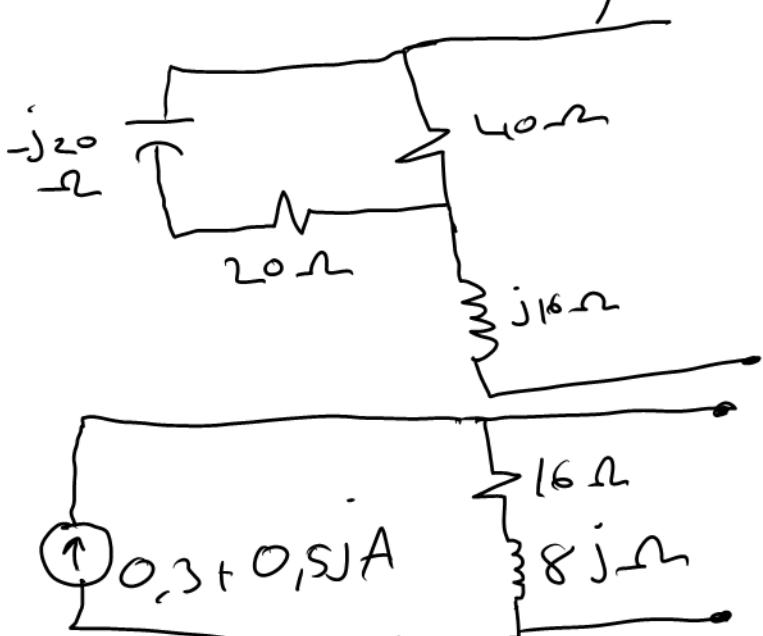
$$-40I_2 + I_N(40 + 16j) - 6.4j + 3.2 = 0 \quad (2)$$




$$Z_N = \frac{(-j20 + 20) // 40 + j16}{(-j20 + 20) \cdot 40} \cdot j16$$

$$= 16 + 8j \Omega$$

9.55 Use the node-voltage method to find the phasor voltage \mathbf{V}_g in the circuit shown in Fig. P9.55.

Figure P9.55

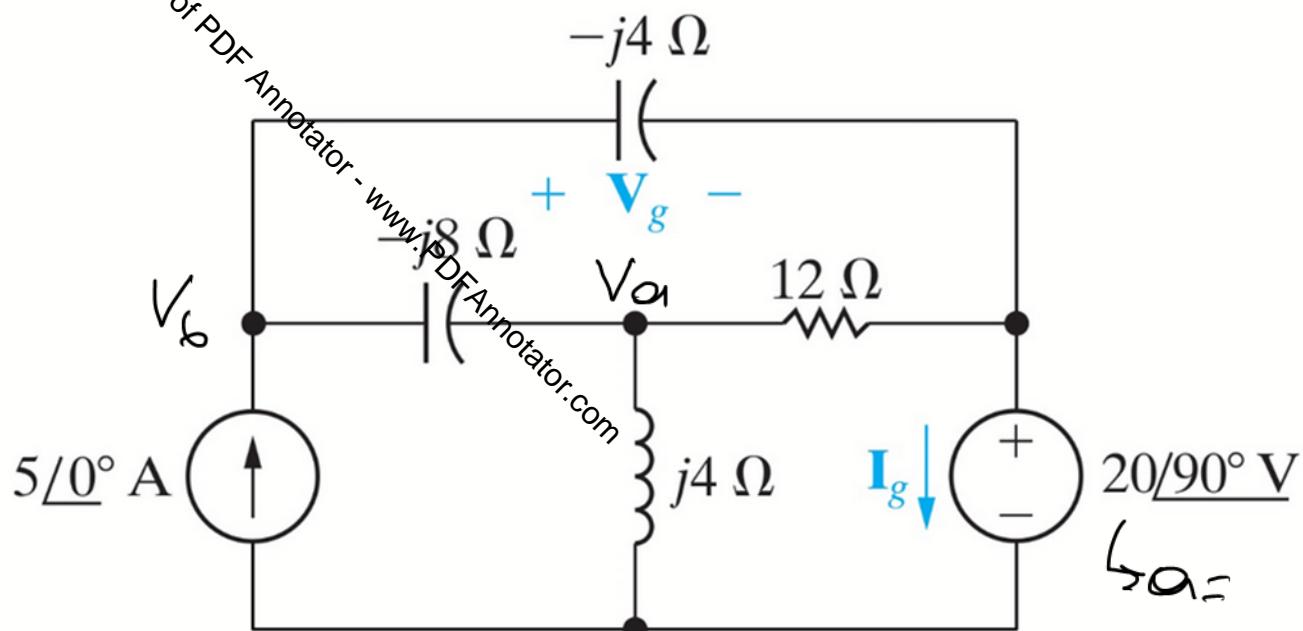

$$-5 + \left(\frac{V_b - V_a}{-j8} \right) + \frac{V_b - 20j}{-j4} = 0$$

$$20\cos(90^\circ) = 0$$

$$b = 20\sin(90^\circ) = 20$$

$$= 20j$$

$$\left(\frac{1}{-j8} + \frac{1}{-j4} \right) V_b + \frac{V_a}{j8} = -5 + 5 \quad (1)$$

I solved this with wolframalpha. eq:

$$((1/(-i^8)+1/(-i^4))^*x + y/(i^8) = 0, (1/(-i^8)+1/(i^4)+1/12)y + x/(8*i) = 5/3i$$

$$\text{Result: } V_b = -8/3 + 4j/3$$

$$V_a = -8+4j$$

$$\frac{V_a - V_b}{-j8} + \frac{V_a}{j4} + \frac{V_a - 20}{12} = 0$$


$$\left(\frac{1}{-j8} + \frac{1}{j4} + \frac{1}{12} \right) V_a - \frac{V_b}{-j8} = \frac{5}{3}j \quad (2)$$

$$V_g = V_b - 20\angle 90^\circ V = -\frac{8}{3} + \frac{4j}{3} - 20j = -\frac{56}{3}j - \frac{8}{3}V$$

Produced with a Trial Version of PDF Annotator - www.PDFAnnotator.com

9.62 Use the mesh-current method to find the branch currents \mathbf{I}_a , \mathbf{I}_b , \mathbf{I}_c , and \mathbf{I}_d in the circuit shown in Fig. P9.62.

Figure P9.62

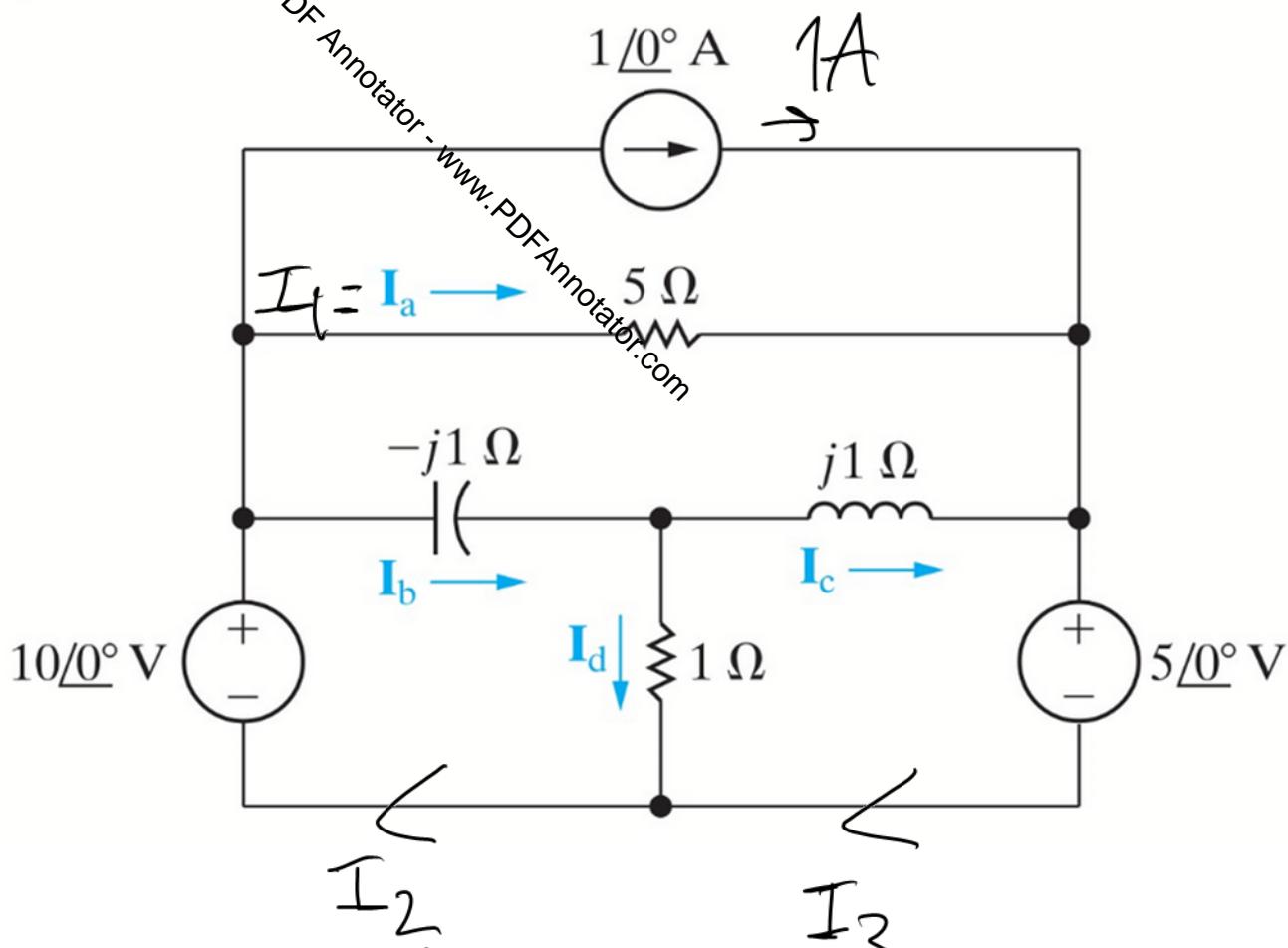

$$5I_1 + j(I_1 - I_3) - j(I_1 - I_2) = 0$$

$$-10 - j(I_2 - I_1) + j(I_2 - I_3) = 0$$

$$5 + (I_3 - I_2) + j(I_3 - I_1) = 0$$

Simplify all three

$$5I_1 + jI_2 - jI_3 = 0 \quad \left. \begin{array}{l} I_1 = 1A \\ I_2 = 6 + 10j \text{ A} \\ I_3 = 6 + 5j \text{ A} \end{array} \right\}$$

$$jI_1 + (-j+1)I_2 - I_3 = 10 \quad \left. \begin{array}{l} I_1 = 1A \\ I_2 = 6 + 10j \text{ A} \\ I_3 = 6 + 5j \text{ A} \end{array} \right\}$$

$$-jI_1 - I_2 + (j+1)I_3 = -5 \quad \left. \begin{array}{l} I_1 = 1A \\ I_2 = 6 + 10j \text{ A} \\ I_3 = 6 + 5j \text{ A} \end{array} \right\}$$

$$I_a = I_1 = 1A \quad I_c = -(I_1 + I_3) = 4 + 5j \text{ A}$$

$$I_b = I_2 - I_1 = 4 + 10j \text{ A} \quad I_d = I_b - I_c = 5j \text{ A}$$