

# **CSE331**

## **Computer Organization**

### **3<sup>rd</sup> Assignment**

### **Report**

**Date**

**19/12/21**

**Author**

Gökbey Gazi Keskin

1901042631

## Table of Contents

Part 1 .....	3
Controller.....	3
Testbench for Multiplier Controller .....	4
Part 2 .....	5
Required Submodules: .....	5
1 – 32 Bit Adder .....	5
2 – 32 Bit XOR Gate .....	5
3 – 32 Bit Subtractor.....	5
4 - 32 Bit Sequential Multiplier (1 <sup>st</sup> part of the Assignment) .....	5
5 – Set Less Than .....	5
6 – 32 Bit NOR Gate.....	6
7 – 32 Bit AND Gate.....	6
8 – 32 Bit OR Gate .....	6
9 – 8x1 32 Bit Multiplexer .....	6
Testbenches for ALU and its submodules: .....	7

# Part 1


I only made the controller part of the Multiplier.

## Controller

Inputs: p0, isDone

Outputs: write, sr, incr

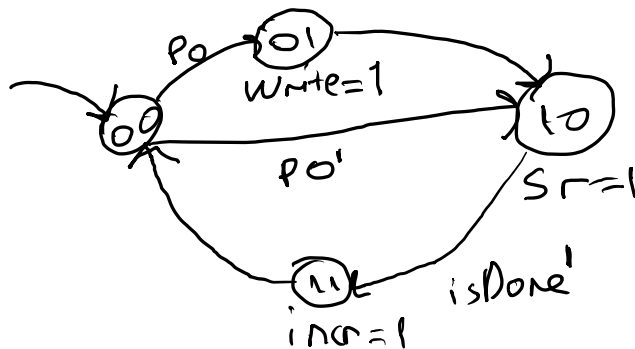I planned to make a counter in datapath and increment it every time incr is 1. When it is 32 isDone should be 1.



S1	S0	p0	isDone	N1	N0	write	sr	incr
0	0	0	X	1	0	0	0	0
0	0	1	X	0	1	0	0	0
0	1	X	X	1	0	1	0	0
1	0	X	0	1	1	0	1	0
1	1	X	X	0	0	0	0	1

N1:

S1S0/p0isDone	00	01	11	10
00	1	1		
01	1	1	1	1
11				
10	1			1

$$s_1' p_0 + s_1' s_0 + s_1 s_0' \text{ isDone'}$$


N0:

S1S0/p0isDone	00	01	11	10
00			1	1
01				
11				
10	1			1

$$s_1' s_0' p_0 + s_1 s_0' \text{ isDone'}$$

write: S1'S0 , sr: S1S0', incr S1S0

## Testbench for Multiplier Controller

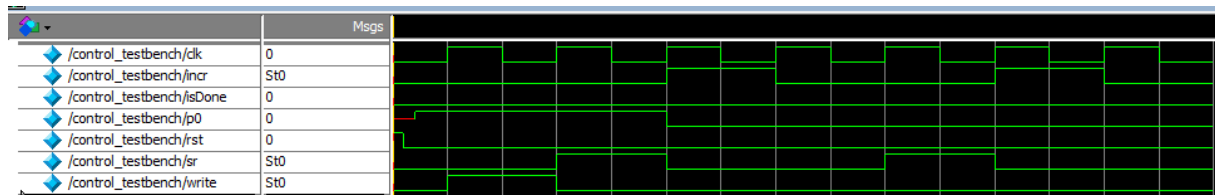

```
# time = 2,p0:1, PS:00 NS:01
# time = 5,p0:1, PS:01 NS:10
# time = 15,p0:1, PS:10 NS:11
# time = 25,p0:0, PS:11 NS:00
# time = 35,p0:0, PS:00 NS:10
# time = 45,p0:0, PS:10 NS:11
# time = 55,p0:0, PS:11 NS:00
# time = 65,p0:0, PS:00 NS:10
```

- next state is 01 when present state is 00 and p0 is 1
- next state is 10 when present state is 00 and p0 is 0
- next state is 10 when present state is 01
- next state is 11 when present state is 10 and isDone is 0
- next state is 00 when present state is 11

Controller works as expected.

## Part 2

### Required Submodules:

#### 1 – 32 Bit Adder

Inputs: A[32], B[32], C0

Outputs: S, Cout, C30 (C30 is used at set less than module to determine if there is an overflow or not  $C_n \text{ XOR } C_{n-1}$  gives the overflow)

I used the full adder given by the T.A of the lecture.

Required Submodule: 1-bit full adder (which requires 1-bit half adder)

#### 2 – 32 Bit XOR Gate

Inputs: A[32], B[32]

Output: R[32]

I XORed inputs bit by bit

#### 3 – 32 Bit Subtractor

Inputs A[32], B[32]

Outputs: R[32], Cout, CnMinus1 (CnMinus1 is used at set less than module to determine if there is an overflow or not  $C_n \text{ XOR } C_{n-1}$  gives the overflow)

Carry in of the 32-bit adder is constant 1. B is reverted by the 32-bit NOT gate which I implemented.

Required Submodules:

-32-bit adder

-32 bit not gate

#### 4 - 32 Bit Sequential Multiplier (1<sup>st</sup> part of the Assignment)

Explained in the first part.

#### 5 – Set Less Than


Inputs: A[32], B[32]

Output: S

Required Submodule: 32-bit subtractor

$S = (\text{cout} \text{ xor } c_{n-1}) \text{ xor } \text{sub}(A,B)[31]$  (isOverflow xor most significant bit of the subtraction)

ALUop	Operation
000	ADD
001	XOR
010	SUB
011	MULT
100	SLT
101	NOR
110	AND
111	OR

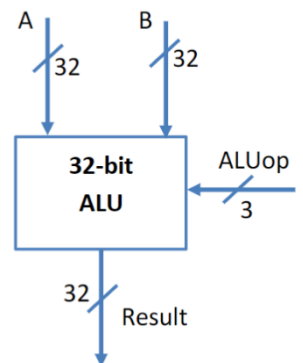

## 6 – 32 Bit NOR Gate

Inputs: A[32], B[32]

Output: R[32]

I NORed inputs bit by bit

## 7 – 32 Bit AND Gate

Inputs: A[32], B[32]

Output: R[32]

I ANDed inputs bit by bit

## 8 – 32 Bit OR Gate

Inputs: A[32], B[32]

Output: R[32]

I ORed inputs bit by bit

## 9 – 8x1 32 Bit Multiplexer

Inputs: A[32], B[32], C[32], D[32], E[32], F[32], G[32], H[32], S[3]


Output: R

First, I made a 2x1 1 bit multiplexer.

$$R = A \text{ and } S' + B \text{ and } S$$

Then, I made a 2x1 32-bit mux by using 32 2x1 1-bit muxes

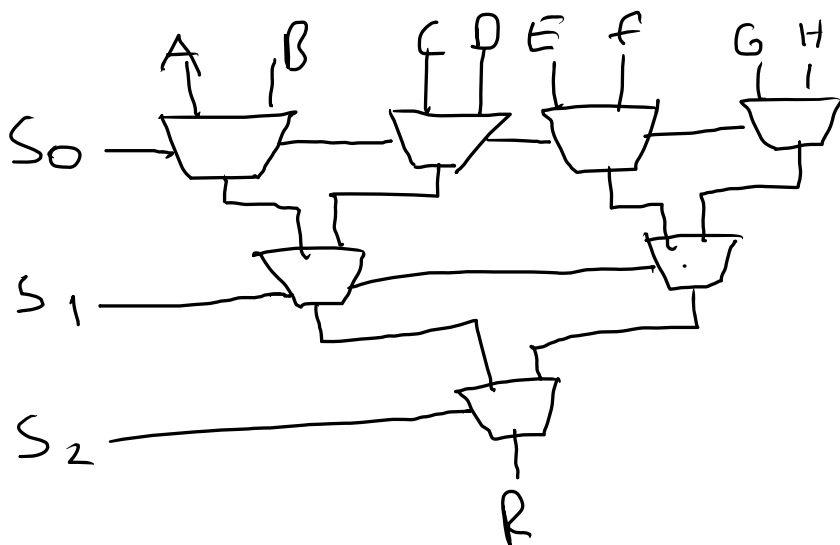Finally, I made an 8x1 32-bit mux by using 7 2x1 32-bit muxes



(All the submodule testbenches are included the file.)

```
# time = 0, a = 10, b= 20, carry_in=0, sum= 30, carry_out=0
# time = 20, a = 15, b= 20, carry_in=0, sum= 35, carry_out=0
# time = 40, a = 0, b= 25, carry_in=0, sum= 25, carry_out=0
# time = 60, a = 10, b= 0, carry_in=0, sum= 10, carry_out=0
# time = 80, a = 12, b= 23, carry_in=0, sum= 35, carry_out=0
# time = 100, a = 70, b= 900, carry_in=0, sum= 970, carry_out=0
# time = 120, a = 100, b= 321, carry_in=0, sum= 421, carry_out=0
# time = 140, a = 222, b= 220, carry_in=1, sum= 443, carry_out=0
# time = 160, a =4000000000, b= 294967296, carry_in=0, sum= 0, carry_out=1
```

# time= 0, a=	10, b=	20, c=	30, d=	40, e=	50, f=	60, g=	70, h=	80,s=0, res=	10
# time=20, a=	10, b=	20, c=	30, d=	40, e=	50, f=	60, g=	70, h=	80,s=1, res=	20
# time=40, a=	10, b=	20, c=	30, d=	40, e=	50, f=	60, g=	70, h=	80,s=2, res=	30
# time=60, a=	10, b=	20, c=	30, d=	40, e=	50, f=	60, g=	70, h=	80,s=3, res=	40
# time=80, a=	10, b=	20, c=	30, d=	40, e=	50, f=	60, g=	70, h=	80,s=4, res=	50
# time=100, a=	10, b=	20, c=	30, d=	40, e=	50, f=	60, g=	70, h=	80,s=5, res=	60
# time=120, a=	10, b=	20, c=	30, d=	40, e=	50, f=	60, g=	70, h=	80,s=6, res=	70
# time=140, a=	10, b=	20, c=	30, d=	40, e=	50, f=	60, g=	70, h=	80,s=7, res=	80

```
# time = 0, a = 10, b= 5, res= 5,
# time = 20, a = 15, b= 3, res= 12,
# time = 40, a = 300, b= 25, res= 275,
# time = 60, a = 123, b= 5, res= 118,
# time = 80, a = 12, b= 12, res= 0,
# time = 100, a = 5, b= 0, res= 5
```

```
# time= 0,a =          10,b=          5,res=0
# time=20,a =          15,b=         20,res=1
# time=40,a =        300,b=         25,res=0
# time=60,a =       123,b=        500,res=1
# time=80,a =         12,b=          0,res=0
# time=100,a =          0,b=         12,res=1
# time=120,a =          7,b=          5,res=0
# time=140,a =          5,b=          7,res=1
# time=160,a =          1,b=          7,res=1
```

[illegible][illegible]

### 32-bit or

```
# time = 0, a = 00000000000011110011101101110, b=0000000000000111001001101100100, res=000000000000111100111111111110
# time = 20, a = 000000000000110010001100001101100, b=00000001001101100001110001101011, res=000000010011111000011000110111
# time = 40, a = 00000000000000000000000000000000, b=1111111111111111111111111111111, res=1111111111111111111111111111
# time = 60, a = 00000000000101000111111111010000, b=00000000000000000000000000000000, res=00000000000101000111111111010000
# time = 100, a = 1111111111111111111111111111111, b=1111111111111111111111111111111, res=1111111111111111111111111111
```

### 32-bit xor

```
# time = 0, a = 00000000000011110011101101110, b=0000000000000111001001101100100, res=0000000000011000000111010111010
# time = 20, a = 000000000000110010001100001101100, b=00000001001101100001110001101011, res=00000001001011110000010000000111
# time = 40, a = 00000000000000000000000000000000, b=1111111111111111111111111111111, res=1111111111111111111111111111
# time = 60, a = 00000000000101000111111111010000, b=00000000000000000000000000000000, res=00000000000101000111111111010000
# time = 100, a = 1111111111111111111111111111111, b=1111111111111111111111111111111, res=00000000000000000000000000000000
```

### 32-bit nor

```
# time = 0, a = 00000000000000000000010100011010110, b=000000000000000111001001101100100, res=11111111111111000100010000001001
# time = 20, a = 000000000000000101000001001110001, b=000000000000000110001101010101011, res=11111111111111000110010100000100
# time = 40, a = 00000000000000000000000000000000, b=1111111111111111111111111111111, res=00000000000000000000000000000000
# time = 60, a = 00000000000101000111111111010000, b=00000000000000000000000000000000, res=111111111111010111000000000101111
# time = 100, a = 1111111111111111111111111111111, b=1111111111111111111111111111111, res=00000000000000000000000000000000
```

### ALU

Test in binary format (for binary operations):

```
# Results:time= 0,a=00000000000000000000000000000000,b=1111111111111111111111111111111,aluOp= 000,res=1111111111111111111111111111111
# Results:time= 20,a=00000000000000010000001111111111,b=00000000000010010101010100100000,aluOp= 000,res=0000000000010100101101100011111
# Results:time= 40,a=000000000000000101100011100011101,b=100100001000010000000110000101101,aluOp= 001,res=10010000100000011000001000010000
# Results:time= 60,a=00000000000000000000000000000000,b=1111111111111111111111111111111,aluOp= 001,res=1111111111111111111111111111111
# Results:time= 80,a=00000000000000000000000000000101,b=000000000000000000000000000001001,aluOp= 010,res=000000000000000000000000000001100
# Results:time= 100,a=000000000000000001000001000111011011,b=000000000000000000000110001111001000,aluOp= 010,res=000000000000011101111111110011
# Results:time= 120,a=0000000000000000000000000000001010,b=00000000000000000000000000000101,aluOp= 011,res=XXXXXXXXXXXXXXXXXXXXXXXXXXXXX
# Results:time= 140,a=000000000000000100101100110011001,b=0000000000000000000000010010010011,aluOp= 100,res=00000000000000000000000000000000
# Results:time= 160,a=0000000000000001100111010110100111,b=00000000000001001011001001001011,aluOp= 100,res=1111111111111111111111111111111
# Results:time= 180,a=000000000000000001011001010111000,b=000000000000000001011000101101101,aluOp= 101,res=1111111111111101000110000000010
# Results:time= 200,a=1111111111111111111111111111111,b=0000000000000000000000000000000000,aluOp= 101,res=00000000000000000000000000000000
# Results:time= 220,a=000000000000010101100010101101101,b=0000000000000000011011010001101100,aluOp= 110,res=000000000000000001000010001101100
# Results:time= 240,a=1111111111111111111111111111111,b=00000000000000000000000000000000,aluOp= 110,res=00000000000000000000000000000000
# Results:time= 260,a=0000000000000101010101011101101,b=000000000000000000000110101011100,aluOp= 111,res=000000000000010101011011111101
# Results:time= 280,a=1111111111111111111111111111111,b=00000000000000000000000000000000,aluOp= 111,res=1111111111111111111111111111111
```

In decimal format(for arithmetic operations):

```
# Results:time= 0,a= 0,b=4294967295,aluOp=0,res=4294967295
# Results:time= 20,a= 5327,b= 1000,aluOp=0,res= 6327
# Results:time= 40,a= 364093,b= 1521517,aluOp=1,res= 1227088
# Results:time= 60,a= 0,b=4294967295,aluOp=1,res=4294967295
# Results:time= 80,a= 53,b= 25,aluOp=2,res= 28
# Results:time= 100,a= 1000,b= 501,aluOp=2,res= 499
# Results:time= 120,a= 10,b= 5,aluOp=3,res= x
# Results:time= 140,a= 1000,b= 3000,aluOp=4,res=4294967295
# Results:time= 160,a= 2000,b= 15,aluOp=4,res= 0
# Results:time= 180,a= 45752,b= 45421,aluOp=5,res=4294921218
# Results:time= 200,a=4294967295,b= 0,aluOp=5,res= 0
# Results:time= 220,a= 705901,b= 111724,aluOp=6,res= 33900
# Results:time= 240,a=4294967295,b= 0,aluOp=6,res= 0
# Results:time= 260,a= 349677,b= 3420,aluOp=7,res= 351741
# Results:time= 280,a=4294967295,b= 0,aluOp=7,res=4294967295
```