
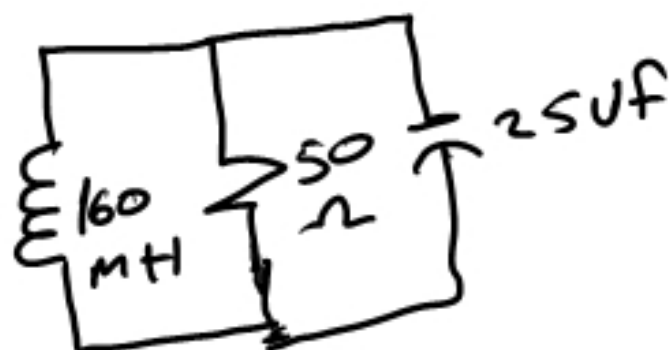
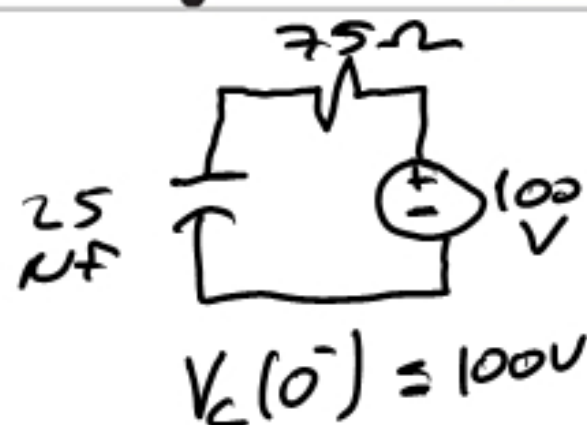
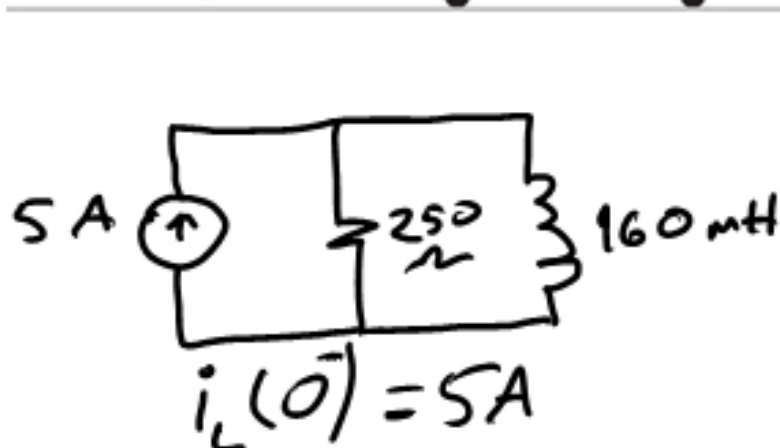


**8.11** The two switches in the circuit seen in Fig. P8.11 operate synchronously. When switch 1 is in position a, switch 2 is in position d. When switch 1 moves to position b, switch 2 moves to position c. Switch 1 has been in position a for a long time. At  $t = 0$ , the switches move to their alternate positions. Find  $v_o(t)$  for  $t \geq 0$ .

Figure P8.11

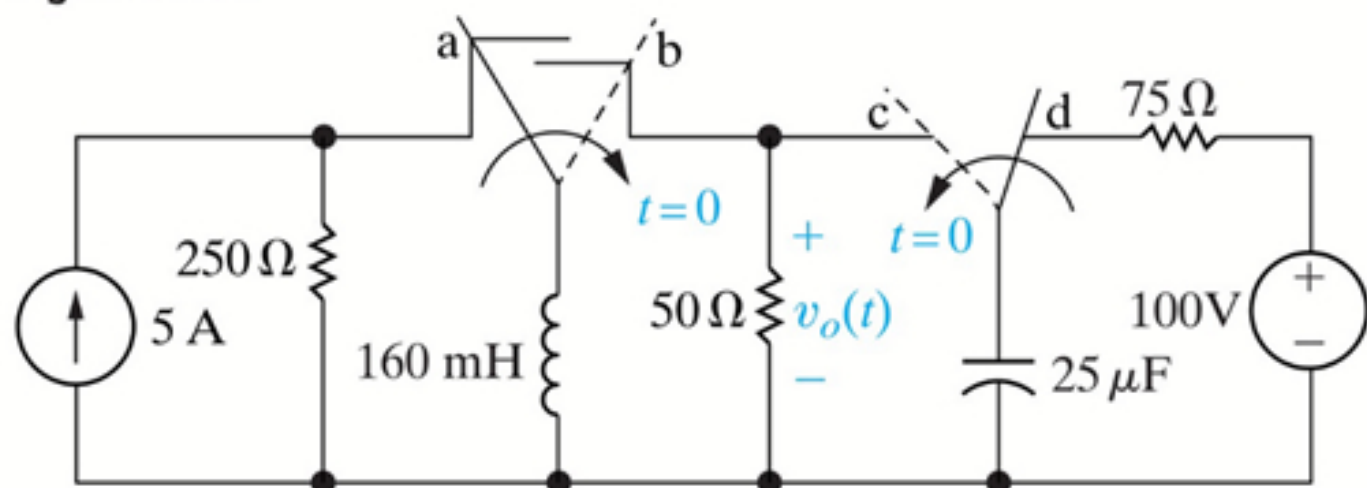

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{160 \times 10^{-3} \cdot 25 \times 10^{-6}}} = 500 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 50 \cdot 25 \times 10^{-6}} = 400 \text{ rad/s}$$

$\omega_0^2 > \alpha^2 \rightarrow \text{under damped}$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 300 \text{ rad/s} \quad B_1 = V_0 = 100 \text{ V}$$

$$i_C(0) = -i_L(0) - i_R(0) = -5 - \frac{100}{50} = -7$$

$$-\alpha B_1 + \omega_d B_2 = \frac{1}{C} \cdot i_C(0)$$

$$-400 \cdot 100 + 300 \cdot B_2 = \frac{1}{25 \cdot 10^{-6}} \cdot -7 \Rightarrow B_2 = -800$$


$$V_o(t) = e^{-\alpha t} \cdot [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)]$$

Insert everything

$$V_o(t) = e^{-400t} \cdot [100 \cos(300t) - 800 \sin(300t)] \text{ V}$$

**8.27** Assume that at the instant the 2 A dc current source is applied to the circuit in Fig. P8.27, the initial current in the 25 mH inductor is 1 A, and the initial voltage on the capacitor is 50 V (positive at the upper terminal). Find the expression for  $i_L(t)$  for  $t \geq 0$  if  $R$  equals 12.5  $\Omega$ .

Figure P8.27

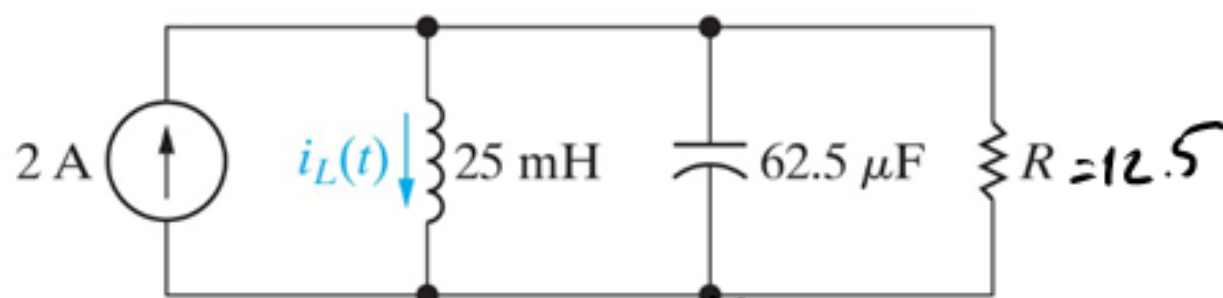

$$i_L(0^-) = 1 \text{ A} \quad V_C(0^-) = 50 \text{ V}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{25 \times 10^{-3} \times 62.5 \times 10^{-6}}} = 800 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 12.5 \times 62.5 \times 10^{-6}} = 640 \text{ rad/s}$$

$$\omega_0^2 > \alpha^2 \quad \text{Underdamped}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 480 \text{ rad/s}$$

$$i_L(t) = e^{-\alpha t} \cdot [B'_1 \cos(\omega_d t) + B'_2 \sin(\omega_d t)] + I_{\infty}$$

$$= B'_1 + I_{\infty} \Rightarrow 1 = B'_1 + 2 \Rightarrow B'_1 = -1$$

$$\frac{V(0)}{L} = -B'_1 \alpha + B'_2 \omega_d \rightarrow \frac{50}{25 \times 10^{-3}} = 640 + 480 B'_2$$


$$\Rightarrow B'_2 = 2.833$$

$$i_L(t) = e^{-640t} \cdot [-1 \cos(480t) + 2.833(480t)] + 2 \text{ A}$$

**8.35** The switch in the circuit in Fig. P8.35 has been in the left position for a long time before moving to the right position at  $t = 0$ . Find


- $i_L(t)$  for  $t \geq 0$ ,
- $v_C(t)$  for  $t \geq 0$ .

Figure P8.35

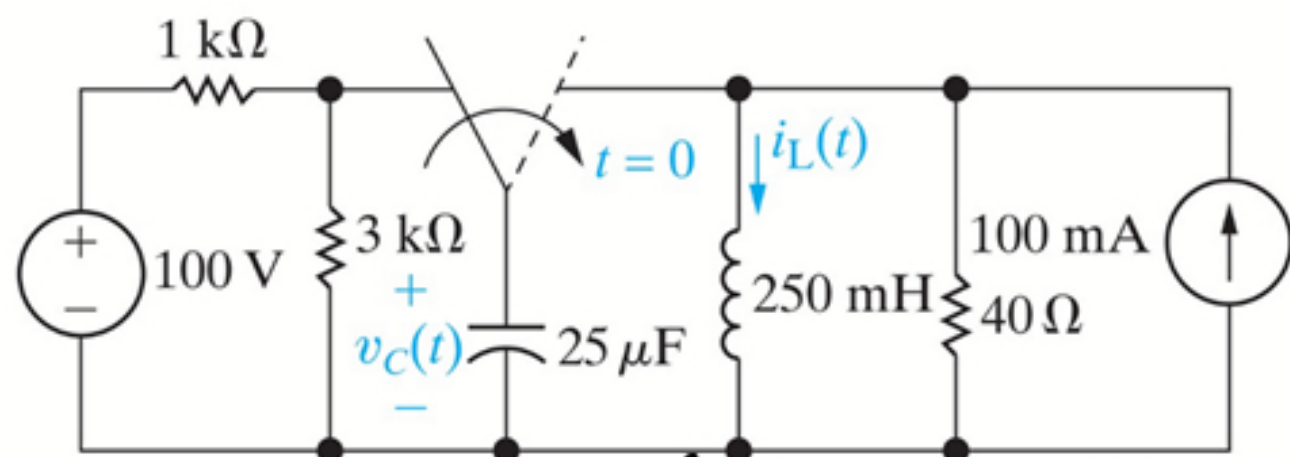

$$V_0 = \frac{3}{4} \cdot 100 = 75$$

$$i_0 = 100 \text{ mA} = 0,1 \text{ A}$$

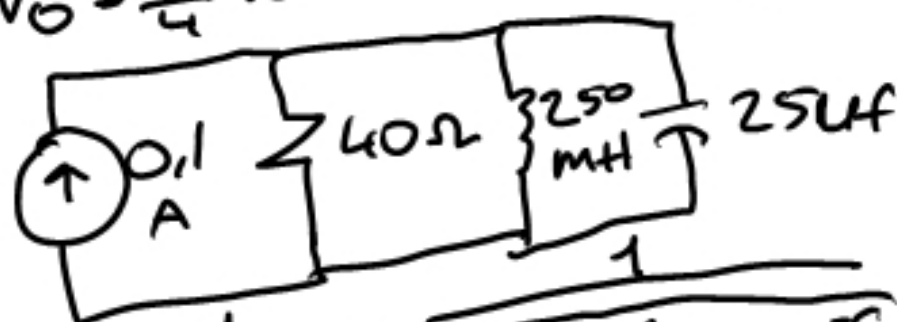

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{250 \times 10^{-3} \times 25 \times 10^{-6}}} = 400 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 40 \cdot 25 \times 10^{-6}} = 500 \text{ rad/s}$$

$$\alpha^2 > \omega_0^2 \text{ Overdamped}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -500 \pm \sqrt{500^2 - 400^2}$$

$$s_1 = -200, s_2 = -800$$

1st eq. for  $t=0$

$$A_1' + A_2' + 0,1 = 0,1$$

$$A_1' + A_2' = 0 \quad / \times 50 +$$

2nd eq. for  $t=0$

$$250 \times 10^{-3} (-200 A_1' - 800 A_2') = 75$$

$$-50 A_1' - 200 A_2' = 75 \Rightarrow A_1' = \frac{1}{2}$$

$$A_2' = -\frac{1}{2}$$

$$i_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + I_f \quad (\text{insert everything})$$

$$i_c(t) = \frac{e^{-200t} - e^{-800t}}{2} + 0,1 \text{ A} \quad (a)$$


$$V_c(t) = L(s_1 A_1 e^{s_1 t} + s_2 A_2 e^{s_2 t}) \quad (\text{insert everything})$$

$$V_c(t) = 250 \times 10^{-3} \cdot (-200 \cdot 0,5 \cdot e^{-200t} - 800 \cdot 0,5 \cdot e^{-800t})$$

$$= 0,25 \cdot (-100e^{-200t} - 400e^{-800t}) = \frac{-25e^{-200t} - 100e^{-800t}}{(b)} \text{ V}$$

**8.47** The switch in the circuit shown in Fig. P8.47 has been closed for a long time. The switch opens at  $t = 0$ . Find  $v_o(t)$  for  $t \geq 0^+$ .

Figure P8.47

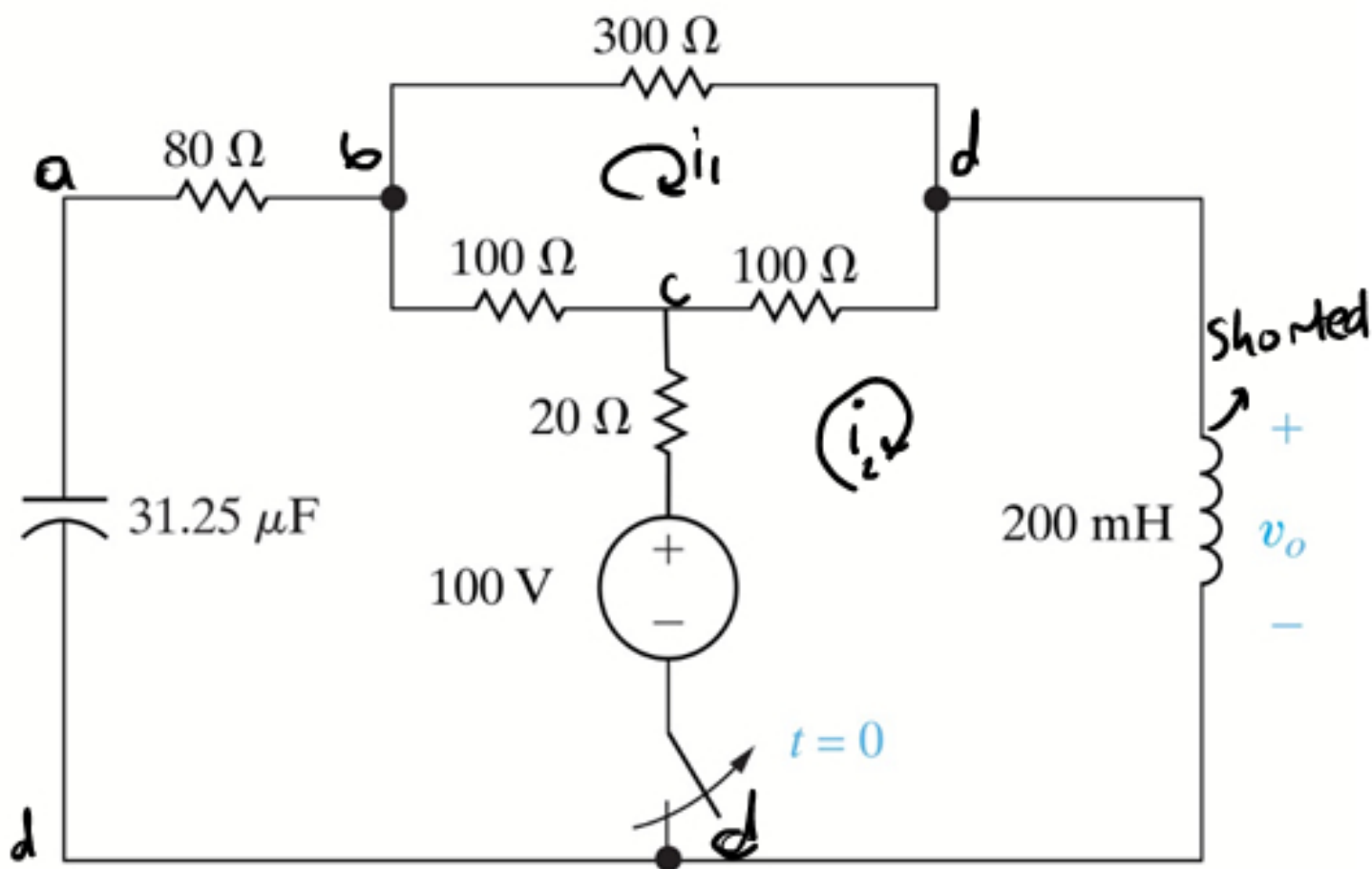



$$\left. \begin{aligned} 300i_1 + 100(i_1 - i_2) + 100i_1 &= 0 \\ -100V + 20i_2 + 100(i_2 - i_1) &= 0 \end{aligned} \right\} \begin{aligned} i_1 &= 0,2A \\ i_2 &= 1A \end{aligned}$$

$$* V_c(0) = V_{ad} = V_{cd} = -100 + 20 \cdot 1 + 100 \cdot 0,2 = \underline{-60V}$$

$$R_{eq}(t > 0) = (300 \parallel (100 + 100)) + 80 = 200 \Omega$$



$$\alpha = \frac{200}{2 \cdot 0,2} = 500 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{0,2 \times 31,25 \times 10^{-6}}} = 400 \text{ rad/s}$$

$\alpha^2 > \omega_0^2$  overdamped

$$* s_1, s_2 = -500 \pm \sqrt{500^2 - 400^2} \Rightarrow \begin{aligned} s_1 &= -200 \\ s_2 &= -800 \end{aligned}$$

$$i_0 = i_2 = 1 = A_1 + A_2 \quad (1)$$

$$L \cdot \frac{di_L(0)}{dt} = V_c(0) = -60 = (A_1 \cdot -200 + A_2 \cdot -800) \cdot 0,2$$

$$3 = -2A_1 - 8A_2 \quad (2) \quad 2 \cdot (1) + (2) \Rightarrow A_1 = \frac{1}{6}, A_2 = \frac{5}{6}$$


$$V_0(t) = L \cdot \frac{di_L(t)}{dt} = (A_1 s_1 \cdot e^{s_1 t} + A_2 s_2 \cdot e^{s_2 t}) \cdot L$$

$$= \left( \frac{-200 \cdot e^{-200t} - 5 \cdot 800 \cdot e^{-800t}}{6} \right) \cdot 0,2$$


$$= 6,67 \cdot e^{-200t} - 133 \cdot e^{-800t} \quad V$$

- 8.54** The two switches in the circuit seen in Fig. P8.55 operate synchronously. When switch 1 is in position a, switch 2 is closed. When switch 1 is in position b, switch 2 is open. Switch 1 has been in position a for a long time. At  $t = 0$ , it moves instantaneously to position b. Find  $v_c(t)$  for  $t \geq 0$ .


Figure P8.54

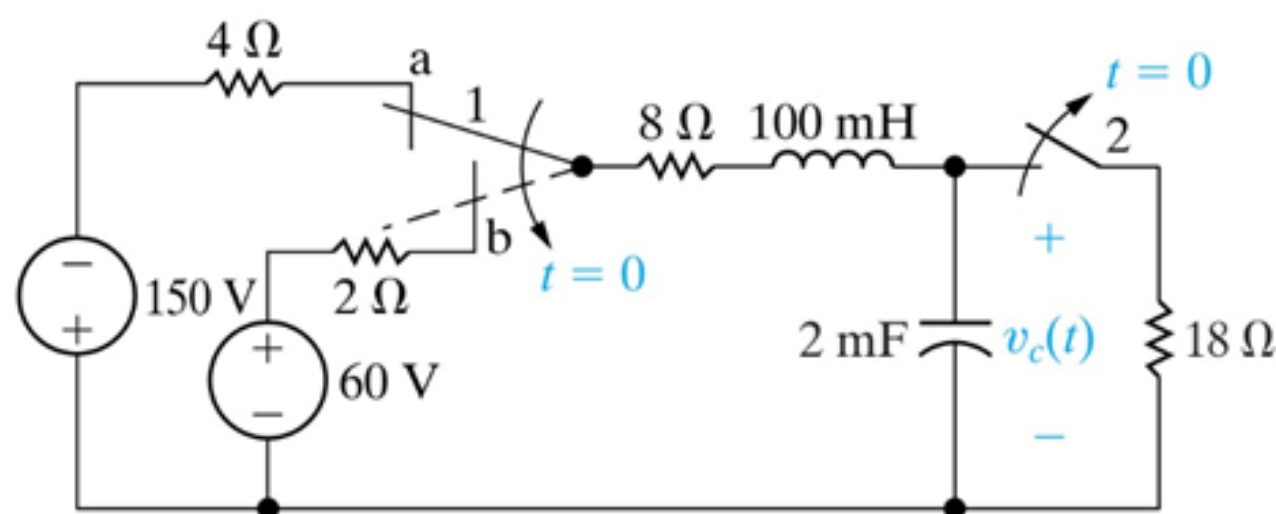

initial:

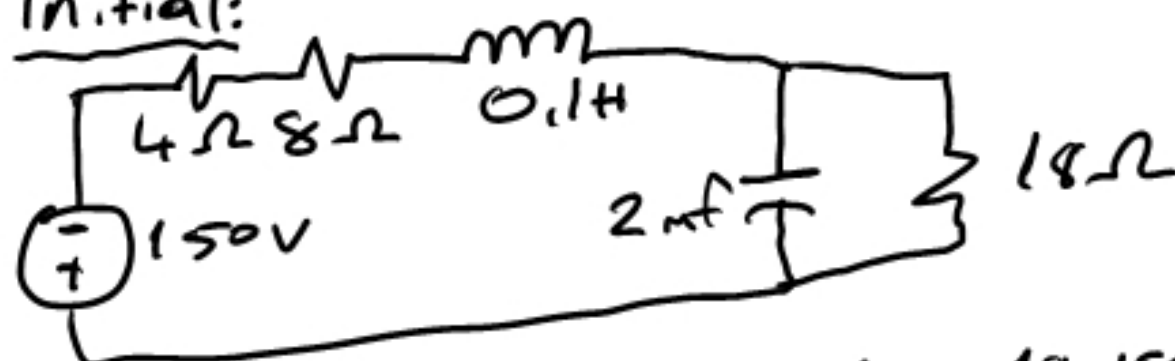

$$-150 = 30 \cdot i_L(0) \Rightarrow i_L(0) = -5A \quad v_c(0) = \frac{18}{30} \cdot -150 = -90V$$

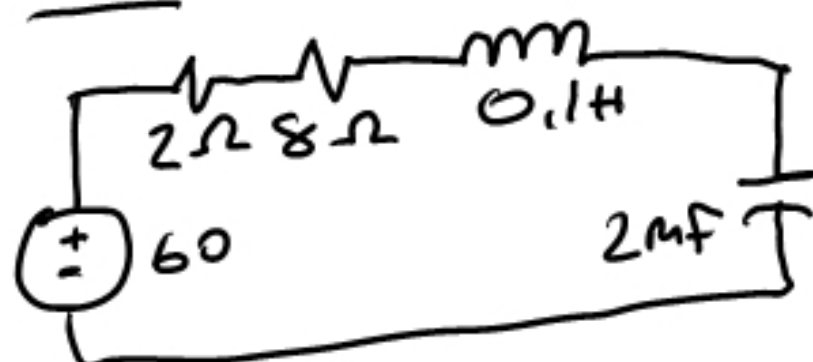 $t > 0$ :

$$R_{eq} = 10\Omega$$





$$V_{-j2\Omega} = 5 \angle 90^\circ \cdot -j2\Omega = 5 \cos(90) + 5 \sin(90)j \cdot -j2\Omega$$

$$= 55 \cdot -j2 = -10j^2 = \underline{\underline{10V}}$$

KVL AT OUTER LOOP:

$$-25 + 10 + (4-j3) \cdot I_+ = 0 \Rightarrow I_+ = \frac{15}{4-j3} \cdot \frac{4+j3}{4+j3} = 2,4 + 1,8jA$$

$$I_b = I_+ - I_q = 2,4 + 1,8j - 5j = \underline{\underline{2,4 - 3,2jA}}$$

KVL AT LOOP 1:

$$-V_b + I_b \cdot (-j5) + I_+ \cdot (-j3 + 4) = 0$$

$$\Rightarrow V_b = \underbrace{(2,4 - 3,2j) \cdot (-j5)}_{-12j - 16} + \underbrace{(2,4 + 1,8j) \cdot (-j3 + 4)}_{15}$$

$$\Rightarrow V_b = -12j - 1$$

KVL AT LOOP 2:

$$-25 + (1+j3)I_q + (-12j-1) = 0$$

$$I_q = \frac{12j + 26}{3j+1} \cdot \frac{3j-1}{3j-1} = \frac{-36 - 12j + 78j - 26}{-9-1} = \frac{60-62}{-10}$$


$$= 6,6j - 6,2A$$

$$I_2 = I_q - I_b = -3,4j + 3,8A$$


$$Z = \frac{-12j-1}{-3,4j+3,8} \cdot \frac{-3,4j-3,8}{-3,4j-3,8} = 1,42 - 1,88j\Omega$$

**9.45** Use source transformations to find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.45.

Figure P9.45

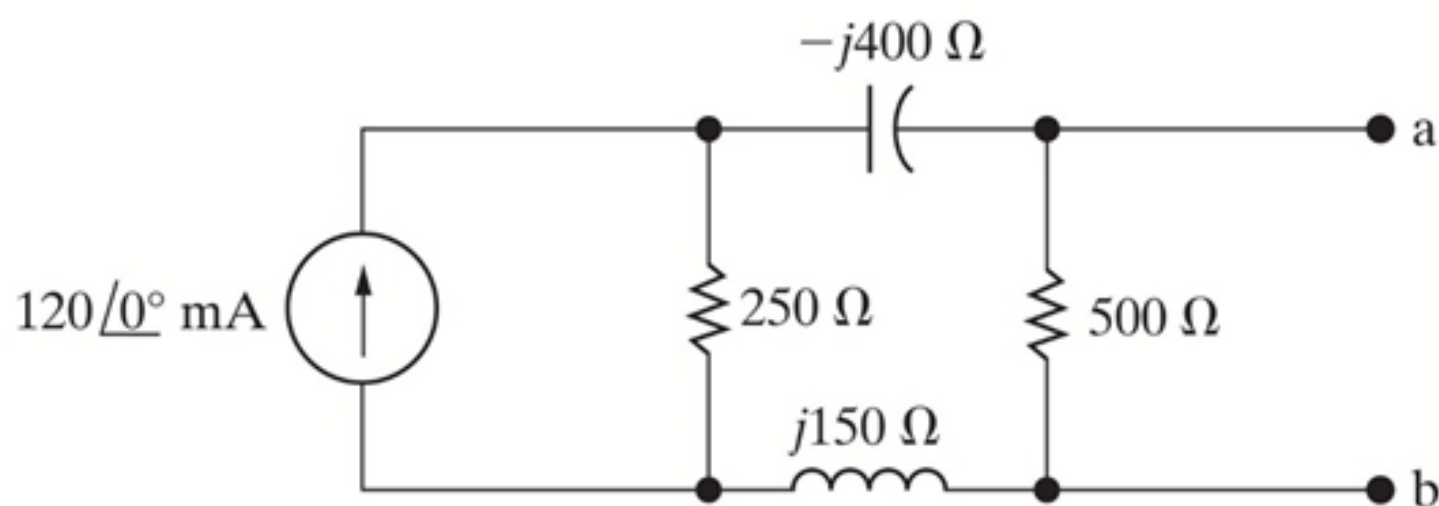
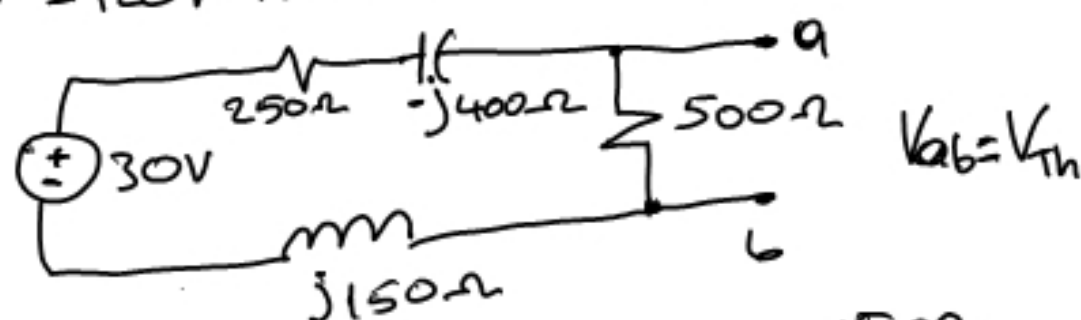
$$V = 120 \text{ mA} \cdot 250 \Omega \Rightarrow V = 30 \text{ V}$$



$$V_{th} = 30 \cdot \frac{500}{500 + 250 + j150 - j400} = \frac{15000}{750 - 250j} = \frac{60}{3 - j} \cdot \frac{-3 - j}{-3 - j}$$

$$= \frac{-180 - 60j}{-10} = 18 + 6j \text{ V}$$


$$Z_{th} = \frac{(250 - j250) \cdot 500}{750 - j250} = \frac{500 - 500j}{3 - j} \cdot \frac{-3 - j}{-3 - j} = \frac{-1000 - 2000j}{-10}$$

$$= -100j + 200 \Omega$$



**9.46** Find the Norton equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.46.

Figure P9.46

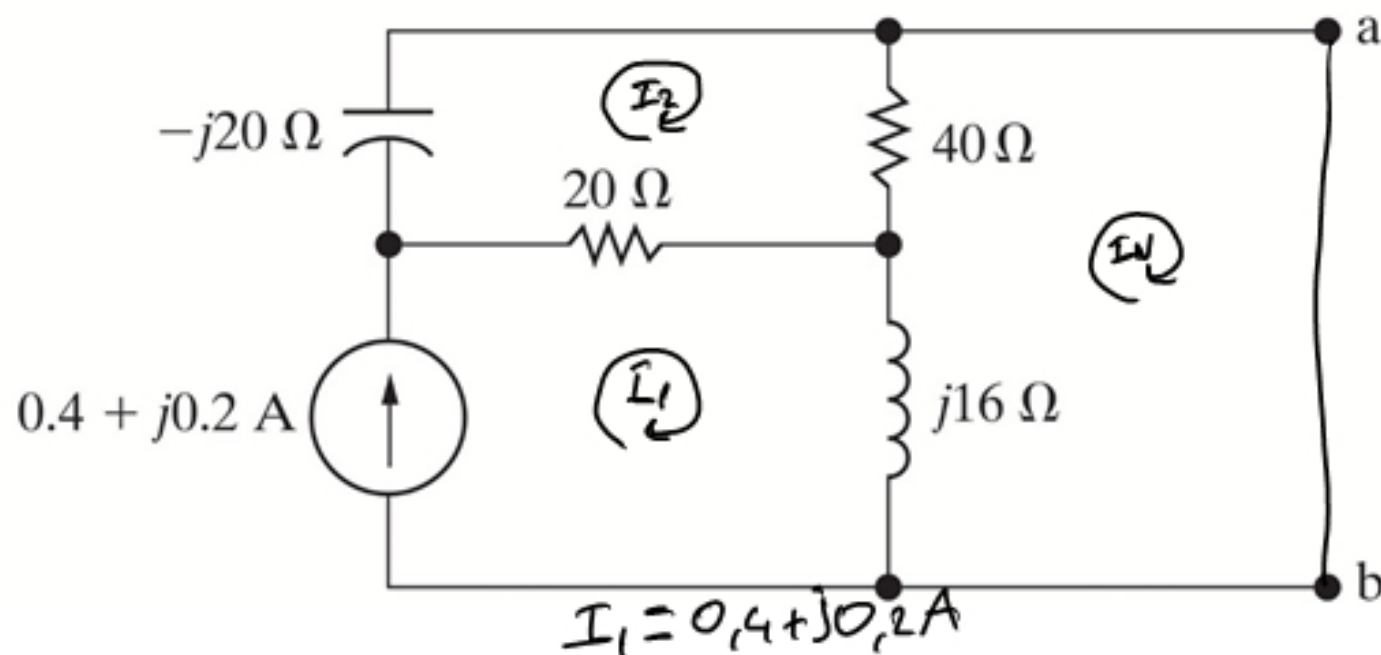

$$I_2(20j) + (I_2 - I_N) \cdot 40 + (I_2 - 0.4 - j0.2) \cdot 20 = 0$$


$$I_2(60 - 20j) - 40I_N - 8 - 4j = 0 \quad (1)$$

Solved this with  
wolf from alpha

$$I_N = 0.3 + j0.5 \text{ A}$$

$$(I_N - 0.4 - j0.2) \cdot 16j + (I_N - I_2) \cdot 40 = 0$$
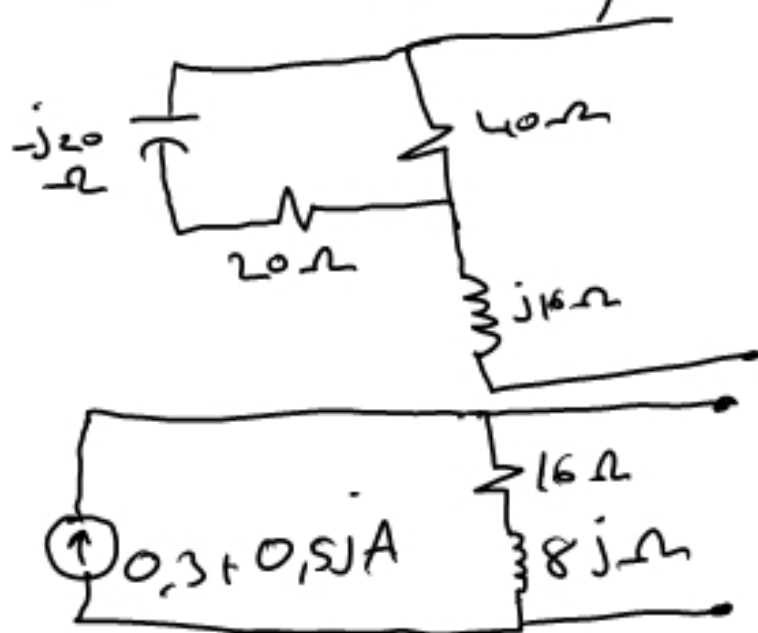
$$-40I_2 + I_N(40 + 16j) - 6.4j + 3.2 = 0 \quad (2)$$




$$Z_N = \left[ (-j20 + 20) \parallel 40 \right] + j16$$

$$= \frac{(-j20 + 20) \cdot 40}{-j20 + 60} + j16$$

$$= 16 + 8j \, \Omega$$

**9.55** Use the node-voltage method to find the phasor voltage  $\mathbf{V}_g$  in the circuit shown in Fig. P9.55.

Figure P9.55

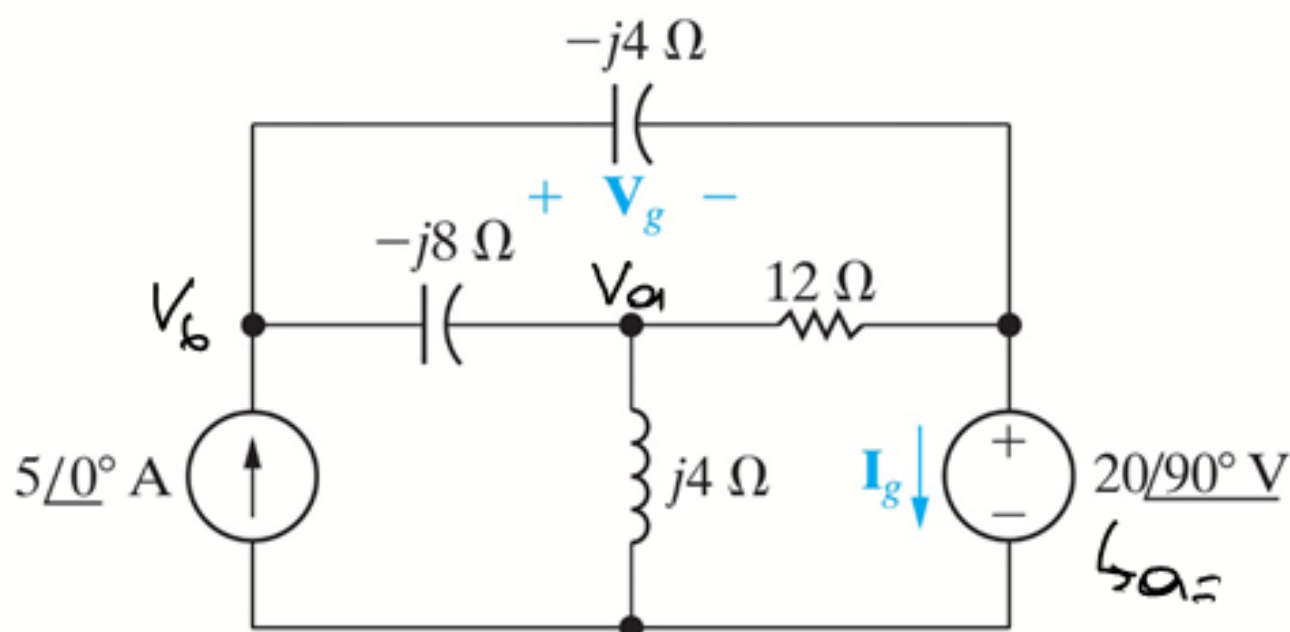

$$\begin{aligned} 20 \cos(90) &= 0 \\ 6 &= 20 \sin(90) = 20 \\ &= 20j \end{aligned}$$

$$-5 + \left( \frac{V_b - V_a}{-j8} \right) + \frac{V_b - 20j}{-j4} = 0$$

$$\left( \frac{1}{-j8} + \frac{1}{-j4} \right) V_b + \frac{V_a}{j8} = -5 + 5 \quad (1)$$

$$\frac{V_a - V_b}{-j8} + \frac{V_a}{j4} + \frac{V_a - 20j}{12} = 0$$

I solved this with wolframalpha. eq:

$$\begin{aligned} ((1/(-j8)) + 1/(-j4))x + \\ y/(j8) = \\ 0, (1/(-j8)) + 1/(j4) + 1/12)y + \\ x/(8j) = 5/3 \end{aligned}$$


$$\begin{aligned} \text{Result: } V_b &= -8/3 + 4j/3 \\ V_a &= -8 + 4j \end{aligned}$$

$$\left( \frac{1}{-j8} + \frac{1}{j4} + \frac{1}{12} \right) V_a - \frac{V_b}{-j8} = \frac{5}{3}j \quad (2)$$

$$V_g = V_b - 20\angle 90^\circ V = -\frac{8}{3} + \frac{4j}{3} - 20j = -\frac{56}{3}j - \frac{8}{3} V$$

**9.62** Use the mesh-current method to find the branch currents  $\mathbf{I}_a$ ,  $\mathbf{I}_b$ ,  $\mathbf{I}_c$ , and  $\mathbf{I}_d$  in the circuit shown in Fig. P9.62.

Figure P9.62

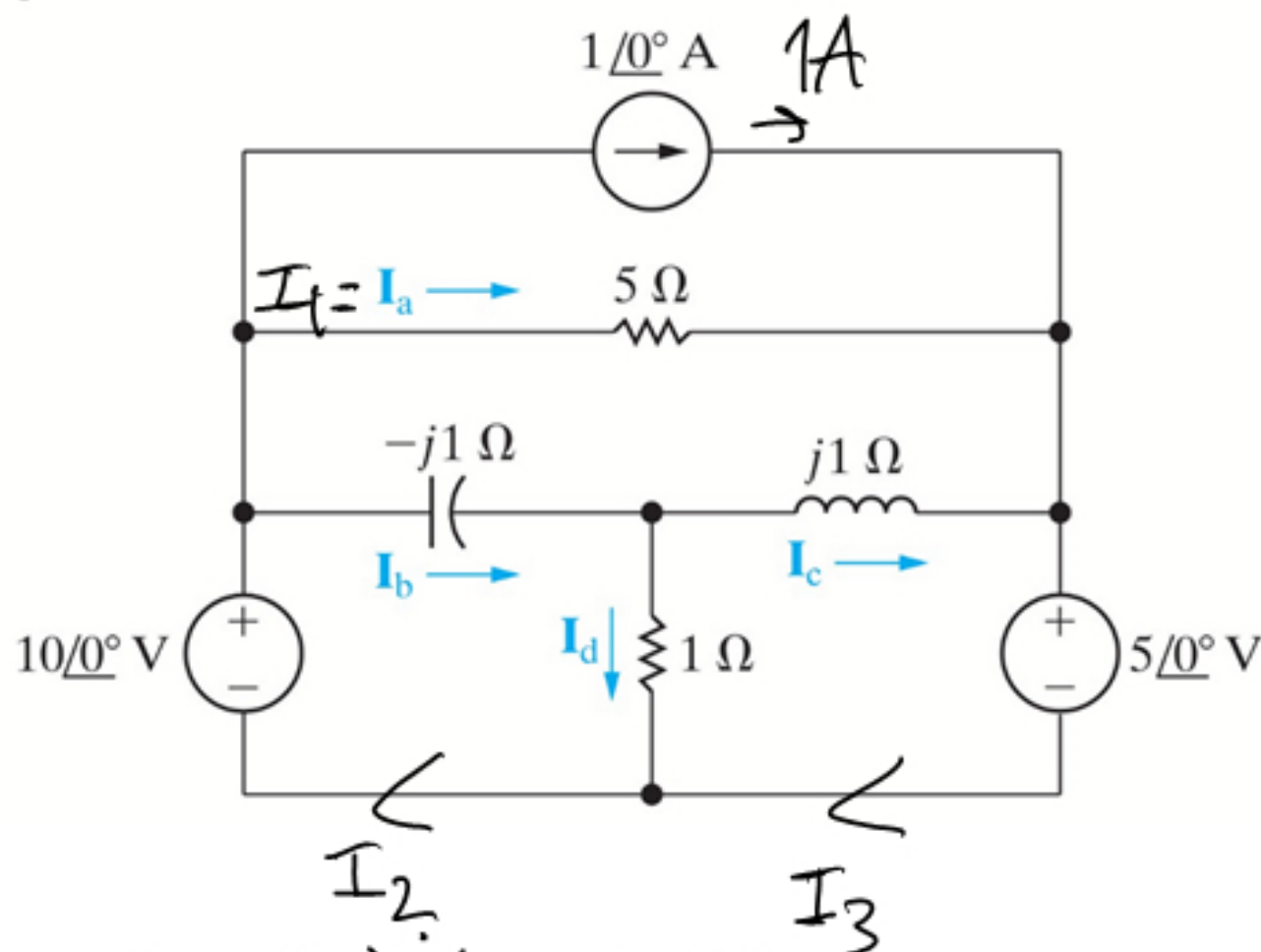

$$5I_1 + j(I_1 - I_3) - j(I_1 - I_2) = 0$$

$$-10 - j(I_2 - I_1) + (I_2 - I_3) = 0$$

$$5 + (I_3 - I_2) + j(I_3 - I_1) = 0$$

simplify all three

$$5I_1 + jI_2 - jI_3 = 0$$

$$jI_1 + (-j+1)I_2 - I_3 = 10$$

$$-jI_1 - I_2 + (j+1)I_3 = -5$$

$$\left. \begin{array}{l} I_1 = 1A \\ I_2 = 6 + 10j A \\ I_3 = 6 + 5j A \end{array} \right\}$$

$$I_a = I_1 = 1A \quad I_c = -(I_1 - I_3) = 4 + 5jA$$

$$I_b = I_2 - I_1 - 1 = 4 + 10jA \quad I_d = I_b - I_c = 5jA$$