

nodes: a, b, c, d, e, f, g 7 nodes. (e)
 branches: a-b, a-d, (a-g), b-e, b-c, b-f
 c-g, d-e, d-g, e-g, af, (a-g)
12 branches. (a)

branches with unknown currents: all except
 25mA current source 11 branches (b)

essential nodes: a, b, d, e, g meshes: 6 meshes. (g)
5 nodes. (f)

essential branches: (a-b), a-d, (a-g), d-g, e-g, b-e, d-e, (a-g), (a-b)
 $(5i\Delta)$ (25mA) $(b-g)$ $(a-b)$
 $(b-g)$ $(28, 2V)$ 10 essential branches. (c) (R_1) $(R_1 + R_2)$


essential branches with unknown currents: all except the one with 25mA current source. 9 essential branches. (d)

4.2) a) Number of essential nodes with unknown currents is the number of needed equations. 9 equations.

b) essential nodes - 1 = 4 eq. can be derived with KCL
 \hookrightarrow reference node

c) $9 - 4 = 5$ eq. must be derived with KVL

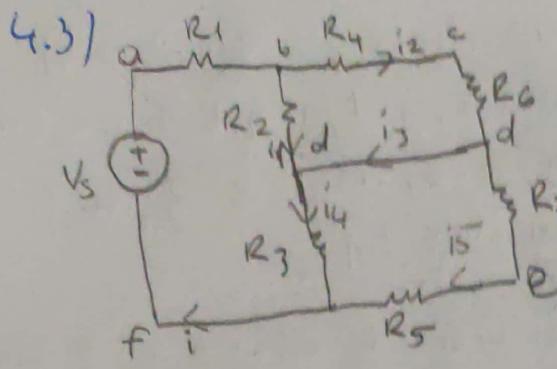d) mesh 2 and 3 should be avoided since we cant determine their voltage drop because they have current sources.



a) 5 unknown current

b) 3 essential nodes (b, d, f) $3 - 1 = 2 \text{ eq}$

$$b: -i + i_1 + i_2 = 0$$

$$f: +i - i_4 - i_5 = 0$$

$$d) 5 - 2 = 3 \text{ eq}$$

$$e) -V_s + i \cdot R_1 + i_1 \cdot R_2 + i_4 \cdot R_3 = 0 \quad (1)$$

$$i_2 (R_4 + R_6) - i_1 \cdot R_2 = 0 \quad (2)$$

$$i_5 (R_7 + R_5) - i_4 \cdot R_3 \quad (3)$$

$$4.4) a) -i + i_2 + i_1 = 0 \quad (b)$$

$$-i_2 - i_1 + i_4 + i_5 = 0 \quad (d)$$


$$-i_5 - i_4 + i = 0 \quad (f)$$

b) sum (b) and (f)

$$i_1 + i_2 + i_1 - i_5 - i_4 + i = 0$$

multiply with (-1) (both sides)
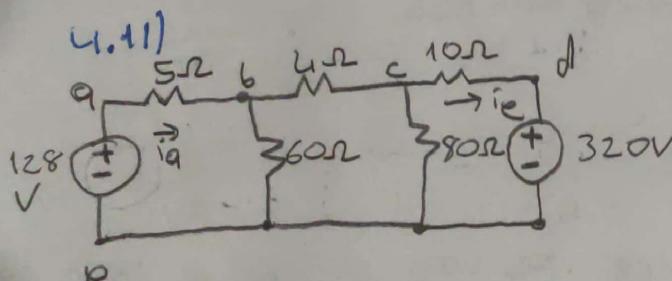
$$\underline{\underline{(b) + (f)}} = \underline{\underline{(d)}} = 0$$



a) reference node: e

$$b: \frac{V_b - V_c}{4} + \frac{V_b}{60} + \frac{V_b - 128}{5} = 0 \quad (60)$$

$$c: \frac{V_c - V_b}{4} + \frac{V_c}{80} + \frac{V_c - 320}{10} = 0 \quad (90)$$

$$15V_b - 15V_c + V_b + 12V_b - 1536 = 0$$

$$28V_b - 15V_c = 1536 \Rightarrow V_b = \frac{1536 + 15V_c}{28}$$

$$-20V_b + 29V_c = 2560$$

$$20V_c - 20V_b + V_c + 8V_c - 2560$$

$$-20\left(\frac{1536 + 15V_c}{28}\right) + 29V_c = 2560$$

$$\Rightarrow -\frac{5}{7}(1536 + 15V_c) + 29V_c = 2560$$

$$\Rightarrow -5(1536 + 15V_c) + 203V_c = 17920$$


$$\Rightarrow 128V_c = 25600 \Rightarrow V_c = \frac{200V}{V_b} = \frac{1536 + 15 \cdot 200}{28} = 162V$$

$$i_a = \frac{128 - 162}{5} = -6,8A$$

$$i_e = \frac{200 - 320}{10} = -12A$$

$$4.111b) P_{144V} = -128 \cdot 6,8 = 870,4W \text{ (absorbed)}$$
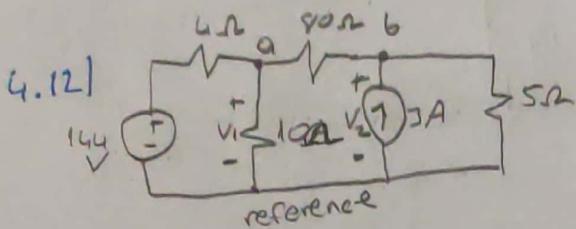
$$P_{320V} = 320 \cdot -12 = 3840W \text{ (developed)}$$



$$a) \frac{V_1 - 144}{4} + \frac{V_1}{10} + \frac{V_1 - V_2}{80} = 0$$

$$b) -3 + \frac{V_2}{5} + \frac{V_2 - V_1}{80} = 0$$


$$a) 20V_1 - 2880 + 8V_1 + V_1 - V_2 = 0$$

$$V_2 = 29V_1 - 2880$$

$$b) -3 + \frac{29V_1 - 2880}{5} + \frac{28V_1 - 2880}{80} = 0$$

$$\Rightarrow -240 + 464V_1 - 46080 + 28V_1 - 2880 = 0$$
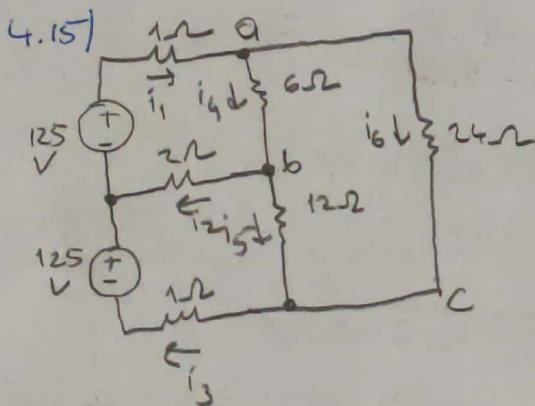
$$\Rightarrow 492V_1 = 49200 \Rightarrow V_1 = 100V \quad V_2 = 29 \cdot 100 - 2880 = 20V$$



$$a) \frac{V_a - 125}{1} + \frac{V_a - V_b}{6} + \frac{V_a - V_c}{24} = 0$$

$$24V_a - 3000 + 4V_a - 4V_b + V_a - V_c = 0$$

$$\textcircled{1} \quad 29V_a - 4V_b - V_c = 3000$$

$$b) \frac{V_b}{2} + \frac{V_b - V_a}{6} + \frac{V_b - V_c}{12} = 0$$

$$6V_b + 2V_b - 2V_a + V_b - V_c = 0$$

$$\textcircled{2} \quad 9V_b - 2V_a - V_c = 0$$

$$c) \frac{V_c + 125}{1} + \frac{V_c - V_b}{12} + \frac{V_c - V_a}{24} = 0$$

$$24V_c + 3000 + 2V_c - 2V_b + V_c - V_a = 0$$

$$\textcircled{3} \quad 27V_c - 2V_b - V_a = -3000$$


$V_a = 101,24V$
$V_b = 10,66V$
$V_c = -106,57V$

$$b) i_1 = \frac{(25 - 101,24)}{1} = 23,76A \quad i_2 = \frac{10,66}{2} = 5,33A \quad i_3 = \frac{-106,57 + 125}{12} = 18,43A$$

$$i_4 = \frac{(101,24 - 10,66)}{6} = 15,097A \quad i_5 = \frac{+10,66 + 106,57}{12} = 9,77A$$

$$i_6 = \frac{101,24 + 106,57}{24} = 8,66A$$

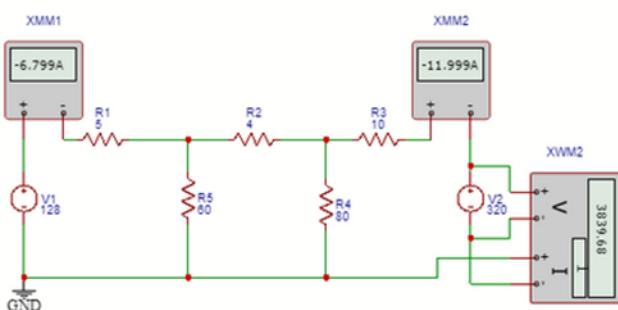
$$P_{\text{developed}} = 125 \cdot 5,33 + 125 \cdot 18,43 = \sum_{n=6}^6 i_n^2 \cdot R_n = 5277,8W$$



4.11

.tran 110m


TITLE:	Sheet_1	REV:	1.0
Company:	Your Company	Sheet:	1/1
EasyEDA	Date: 2020-11-17	Drawn By:	Gökbeý Keskin

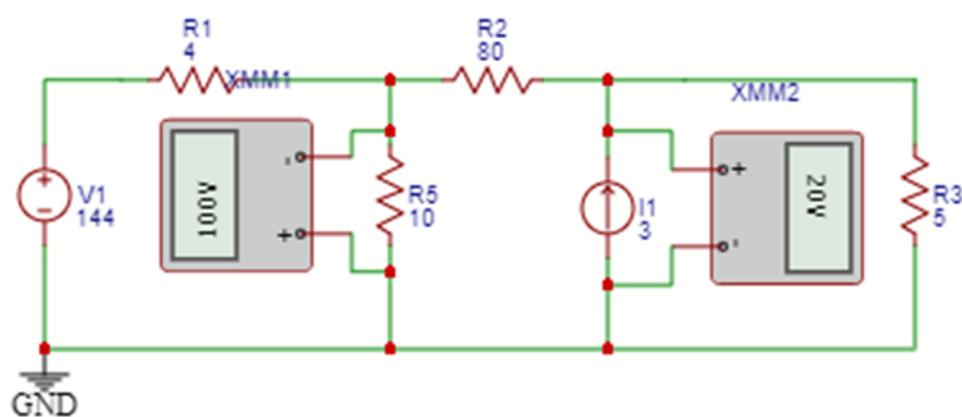

4.12

.tran 110m

TITLE:	Sheet_1	REV:	1.0
Company:	Your Company	Sheet:	1/1
EasyEDA	Date: 2020-11-17	Drawn By:	Gökbeý Keskin

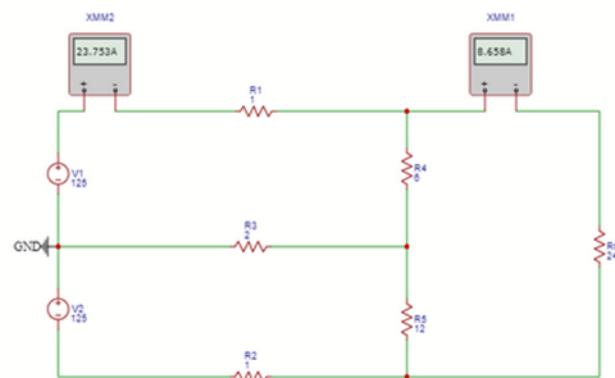


4.15

.tran 10m

*I cant use wattmeter
on evey single element
because it says circuit
is too complicated.
But I checked every element
one at a time, values hold.*

TITLE: Sheet_1		REV: 1.0
Company: Your Company		Sheet: 1/1
EasyEDA		Date: 2020-11-17 Drawn By: Gökbeý Keskin

4.24)

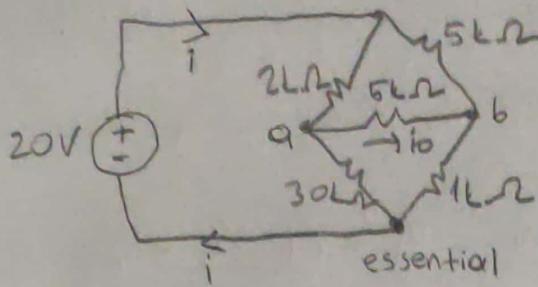

$$\frac{V_a - 20}{2000} + \frac{V_a - V_b}{5000} + \frac{V_a}{3000} = 0$$

$$15V_a - 300 + 6V_a - 6V_b + V_a = 0$$

$$\frac{V_b - 20}{5000} + \frac{V_b - V_a}{5000} + \frac{V_b}{1000} = 0$$

$$22V_b = 300 + 6V_b$$

$$V_b = \frac{150 + 3V_b}{11}$$

$$V_b - 20 + V_b - V_a + 5V_b = 0$$

$$7V_b = V_a + 20$$

$$7V_b = \frac{150 + 3V_b}{11} + 20$$

$$77V_b = 150 + 3V_b + 220$$

$$V_b = 5V$$

$$V_a = \frac{150 + 3.5}{11} = 15V$$


$$i_o = \frac{V_a - V_b}{5000} = \frac{10}{5000} = 2mA$$

$$b) V_{20V} = \frac{20 - V_a}{2000} = 2.5mA$$

$$i = 2.5 + 3 = 5.5mA$$

$$V_{5k\Omega} = \frac{20 - V_b}{5000} = 3mA$$

$$P_{20V} = 20V \cdot 5.5mA = 110mW$$

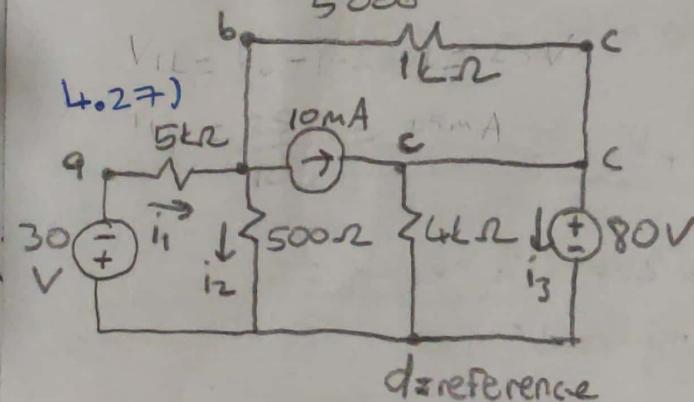

$$V_c = 80V \quad V_a = -30V$$

$$\frac{V_b + 30}{5000} + \frac{V_b}{500} + 0.01 + \frac{V_b - 80}{1000} = 0$$

$$V_b + 30 + 10V_b + 50 + 5V_b - 600 = 0$$


$$16V_b = 320 \quad V_b = 20V$$

$$i_1 = \frac{-30 - 20}{5000} = -0.01A = 10mA$$

$$i_2 = \frac{20}{500} = 0.04A = 40mA$$

$$i_3 = 10mA + \frac{20 - 80}{1000} - \frac{80}{4000} = 0.01 + (-0.06) - 0.02 = 30.07A - 70mA$$
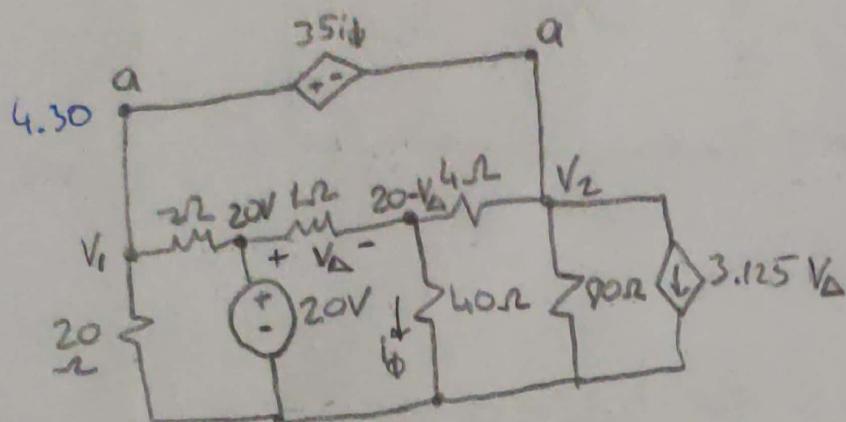
$$4.27) 6 \quad 30 \cdot (-0,01) + 80 \cdot (-0,07) = (-0,01)^2 \cdot 5000 + (0,04)^2 \cdot 500 + \left(\frac{10}{4000}\right)^2 \cdot 4000$$



From the super node:

$$V_1 - 35i_\phi = V_2$$

$$i_\phi = \frac{V_1 - V_2}{35} \quad (1)$$

$$i_\phi = \frac{20 - V_\Delta}{40} \quad (2)$$

for $20 - V_\Delta$:

$$\frac{-V_\Delta}{1} + \frac{20 - V_\Delta}{40} + \frac{20 - V_\Delta - V_2}{4} = 0 \Rightarrow -40V_\Delta + 20 - V_\Delta + 200 - 10V_\Delta - 10V_2 = -51V_\Delta - 10V_2 + 220 = 0 \quad (3)$$

for the super node:

$$\frac{V_1}{20} + \frac{V_1 - 20}{2} + \frac{V_2 - 20 + V_\Delta}{4} + \frac{V_2}{80} + 3,125V_\Delta = 0$$

Put $V_2 + 35i_\phi$ for V_1 and $\frac{20 - V_\Delta}{40}$ for i_ϕ

$$\frac{V_2 + 35\left(\frac{20 - V_\Delta}{40}\right)}{20} + \frac{V_2 + 35\left(\frac{20 - V_\Delta}{40}\right) - 20}{2} + \frac{V_2 - 20 + V_\Delta}{4} + \frac{V_2}{80} + 3,125V_\Delta$$

$$160V_2 + 2800 - 140V_\Delta + 1600V_2 + 28000 - 1400V_\Delta + 800V_2 - 16000 + 800V_\Delta + 40V_2 + 10000 = 0$$

$$22600V_2 - 740V_\Delta = 24800$$

$$\Rightarrow 130V_2 - 37V_\Delta = 1240V$$


$$10V_2 + 51V_\Delta = 220V \quad (3)$$

$$V_2 = -29V \quad V_\Delta = 10V$$

$$V_1 = -20,25V \quad i_\phi = 0,25A$$

$$P_{20V} = \left(\frac{20 - V_1}{2} + \frac{V_\Delta}{1} + \frac{40,25}{2} + 10 \right) \cdot 10$$


$$= 602,5 \text{ mW}$$

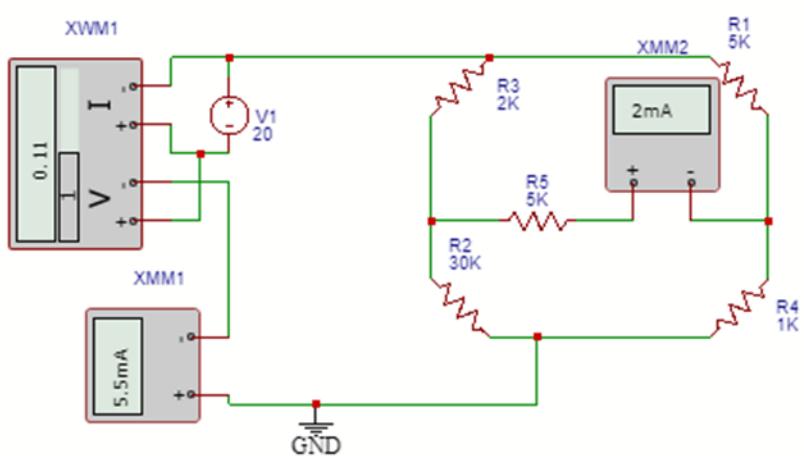

U2L4

.tran 110m


TITLE: Sheet_1		REV: 1.0
	Company: Your Company	Sheet: 1/1
Date: 2020-11-17	Drawn By: Gökbeý Keskin	

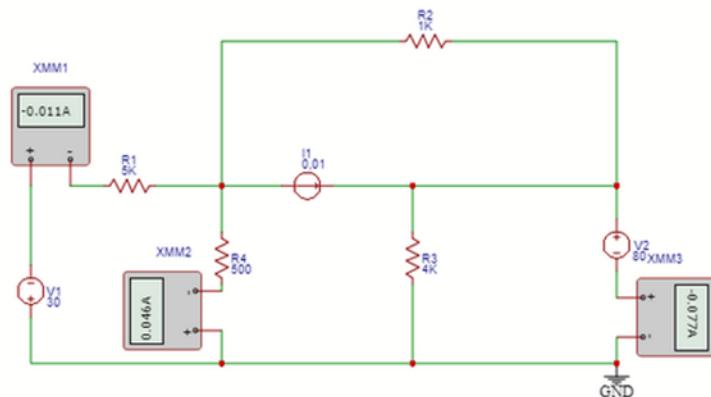

.tran 110m

L27


TITLE:	Sheet_1	REV: 1.0
Company:	Your Company	Sheet: 1/1
EasyEDA	Date: 2020-11-18	Drawn By: Gökbeý Keskin

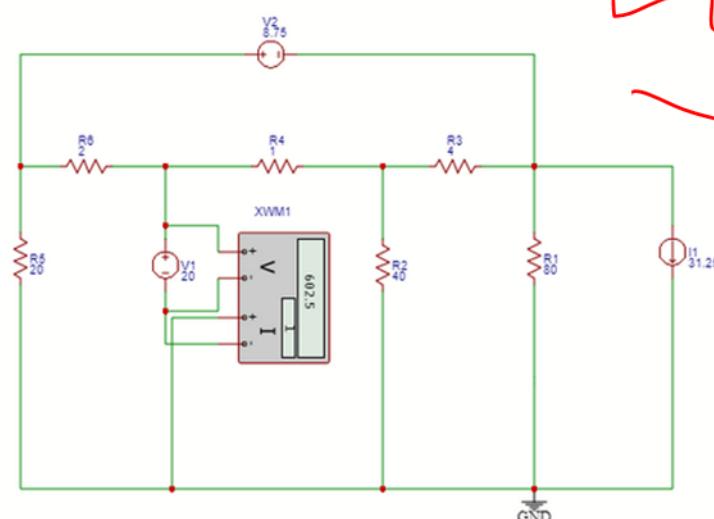

L30

.tran 110m

TITLE:	Sheet_1	REV: 1.0
Company:	Your Company	Sheet: 1/1
EasyEDA	Date: 2020-11-18	Drawn By: Gökbeý Keskin

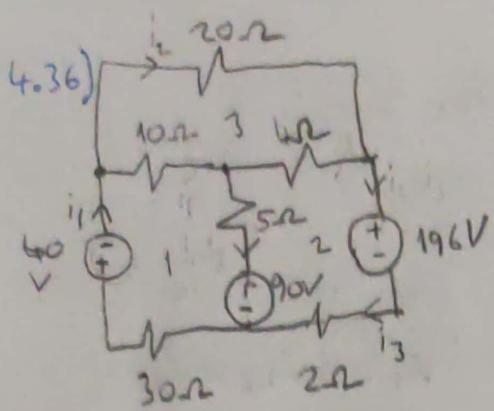

a)

$$40 + (i_1 - i_2) \cdot 10 + (i_1 - i_3) \cdot 5 + 90 + i_1 \cdot 30 = 0 \quad ①$$

$$i_2 \cdot 20 + (i_2 - i_3) \cdot 4 + (i_2 - i_1) \cdot 10 = 0$$

$$i_3 \cdot 2 - 90 + (i_3 - i_1) \cdot 5 + (i_3 - i_2) \cdot 4 + 196 = 0$$

$$45i_1 - 10i_2 - 5i_3 + 130 = 0$$

$$-10i_1 + 34i_2 - 4i_3 = 0 \quad i_1 = -5 \text{ A}$$

$$-5i_1 - 4i_2 + 11i_3 + 166 = 0 \quad i_2 = -3 \text{ A}$$

$$i_3 = -13 \text{ A}$$


$$P_{40V} = 40 \cdot (-5) = -200 \text{ W (delivers)}$$

$$P_{90V} = 90 \cdot (-5 - (-13)) = 720 \text{ W (absorbs)}$$


$$2548 + 200 = \underline{\underline{2748 \text{ W}}}$$

$$P_{196V} = 196 \cdot (-13) = -2548 \text{ W (delivers)}$$
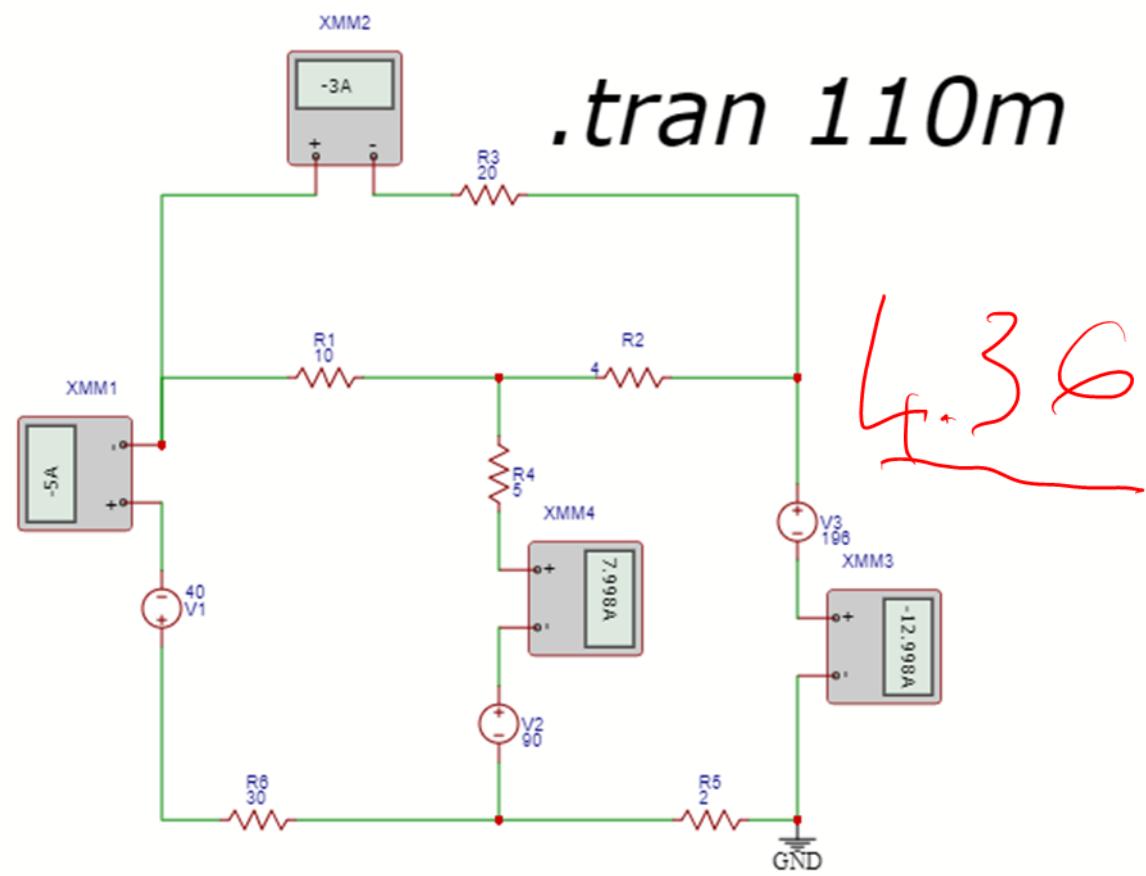
$$\begin{aligned} b) & 30 \cdot 5^2 + 10 \cdot (5 - 3)^2 + 5 \cdot (-5 + 13) 1^2 + 90 \cdot (-5 + 13) + 2 \cdot 13^2 + 4 \cdot (13 - 3)^2 \\ & + 20 \cdot 3^2 = \underline{\underline{2748 \text{ W}}} \end{aligned}$$



TITLE: Sheet_1		REV: 1.0
	Company: Your Company	Sheet: 1/1
	Date: 2020-11-17 Drawn By: Gökbeý Keskin	

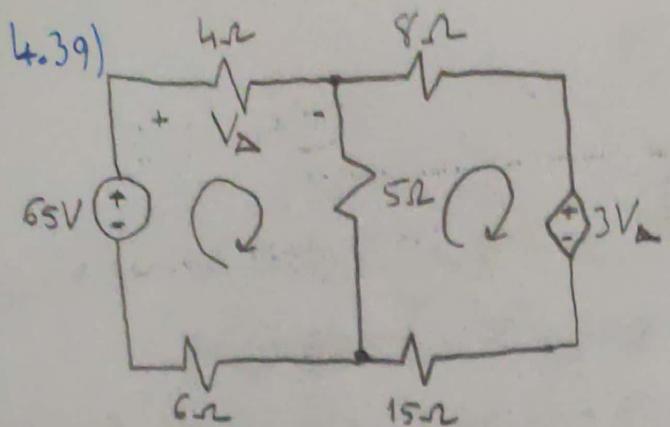

$$V_{\Delta} = i_1 \cdot 4$$

$$-65V + i_1 \cdot 4 + (i_1 - i_2) \cdot 5 + i_2 \cdot 6 = 0$$

$$i_2 \cdot 8 + 3(i_1 \cdot 4) + i_2 \cdot 15 + (i_2 - i_1) \cdot 5 = 0$$

$$15i_1 - 5i_2 = 65$$


$$i_2 = 3i_1 - 13$$

$$28i_2 + 12i_1 - 5i_1 = 0$$

$$28(3i_1 - 13) + 12i_1 - 5i_1 = 0$$

$$91i_1 = 364 \Rightarrow i_1 = 4A \Rightarrow i_2 = 3 \cdot 4 - 13 = -1A$$

$$P_{15\Omega} = (-1)^2 \cdot 15 = 15W$$

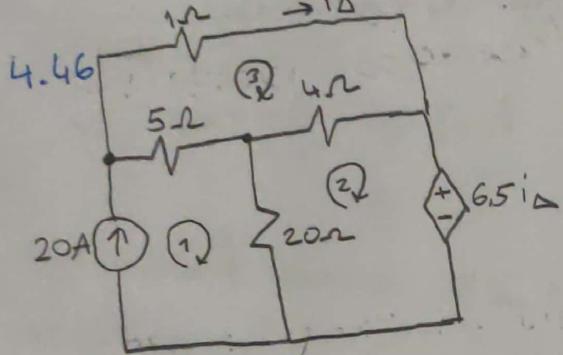

$$i_1 = 20$$

$$6.5i_{\Delta} + (i_2 - 20) \cdot 20 + (i_2 - i_{\Delta}) \cdot 4 = 0$$

$$25i_{\Delta} + 24i_2 = 400 \Rightarrow i_2 = 20 - 5i_{\Delta}$$

$$i_{\Delta} \cdot 1 + (i_{\Delta} - i_2) \cdot 4 + (i_{\Delta} - 20) \cdot 5 = 0$$

$$10i_{\Delta} - 4i_2 = 100$$

$$-4/ 2.5i_{\Delta} + 24i_2 = 400$$

$$\underline{-100i_2 = -1500} \quad \underline{i_2 = 15A}$$

$$2.5i_{\Delta} + 24 \cdot 15 = 400$$


$$\underline{i_{\Delta} = 16A}$$

$$-\sqrt{2} \cdot 20A + (20 - 16) \cdot 5 + (20 - 15) \cdot 20 = 0$$

$$V_{20A} = 120V$$

$$P_{20A} = -(120 \cdot 20) = \underline{-2400W} \text{ (developed)} \quad \underline{2400W}$$

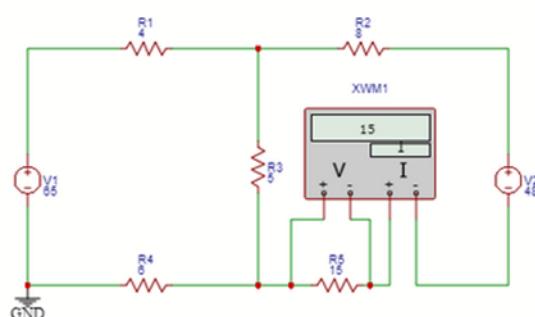
$$P_{6.5i_{\Delta}} = (6.5 \cdot 16) \cdot 15 = \underline{1560W} \text{ (absorbed)}$$



4, 3, 9

.tran 110m

TITLE:	Sheet_1	REV: 1.0
Company:	Your Company	Sheet: 1/1
EasyEDA	Date: 2020-11-18	Drawn By: Gökbeý Keskin

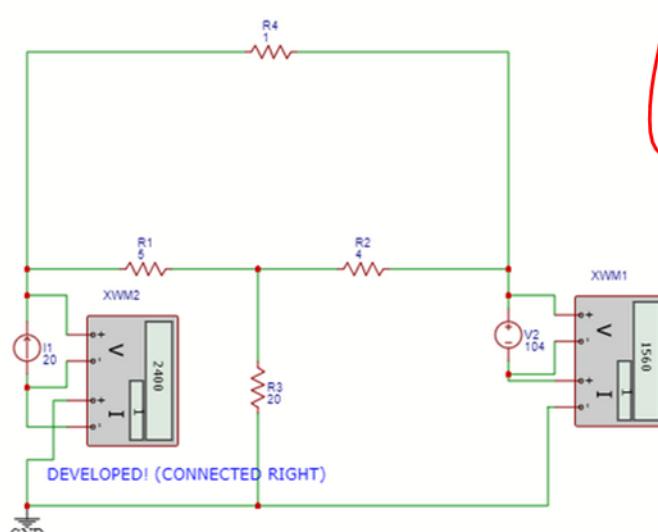

4, 4, 6


.tran 110m

DEVELOPED! (CONNECTED RIGHT)

ABSORBED! (CONNECTED BACKWARDS)

TITLE:	Sheet_1	REV: 1.0
Company:	Your Company	Sheet: 1/1
EasyEDA	Date: 2020-11-18	Drawn By: Gökbeý Keskin

4.47)

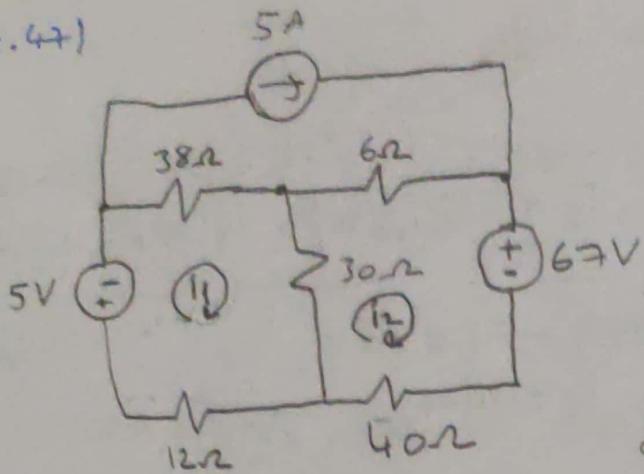

a)

$$i_1 \cdot 12 + 5 \cdot 5 + (i_1 - 5) \cdot 38 + (i_1 - i_2) \cdot 30 = 0$$

$$3 / 80i_1 - 30i_2 = 185 \quad (1)$$

$$67 + i_2 \cdot 40 + (i_2 - i_1) \cdot 30 + (i_2 - 5) \cdot 6 = 0$$

$$8 / -30i_1 + 76i_2 = -37 \quad (2)$$

$$240i_1 - 90i_2 = 555$$

$$-240i_1 + 608i_2 = -296$$

$$518i_2 = 259$$

$$i_2 = 0,5 \text{ A} \Rightarrow 80i_1 - 30 \cdot 0,5 = 185 \Rightarrow i_1 = 2,5 \text{ A}$$

$$-V_{SA} + (5 - 0,5) \cdot 6 + (5 - 2,5) \cdot 38 = 0$$

$$V_{SA} = 12,2 \text{ V} \quad P_{5A} = 122,5 = \underline{\underline{610 \text{ W}}}$$


$$b) P_{5V} = 2,5 \cdot 5 = 12,5 \text{ W} \text{ (absorbs)}$$

$$\underline{\underline{610 \text{ W}}}$$

$$P_{67V} = 0,5 \cdot 67 = 33,5 \text{ W} \text{ (absorbs)}$$

$$c) 12,5 + 33,5 + (2,5)^2 \cdot 12 + (2,5 - 5)^2 \cdot 38 + (2,5 - 0,5)^2 \cdot 30 + (5 - 0,5)^2 \cdot 6 + (0,5)^2 \cdot 40 = \underline{\underline{610 \text{ W}}}$$

4.54)

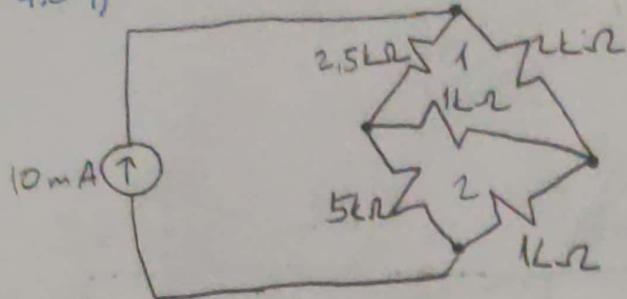

a) I would use mesh-current method because there is only 2 unknown mesh currents but 3 unknown node voltages.

b)

$$i_1 \cdot 2000 + (i_1 - i_2) \cdot 1000 + (i_1 - 0,01) \cdot 2500 = 0$$

$$i_2 \cdot 1000 + (i_2 - 0,01) \cdot 5000 + (i_2 - 1) \cdot 1000 = 0$$

$$5500i_1 - 1000i_2 = 25 \quad | \times 7$$

$$-1000i_1 + 7000i_2 = 50$$

$$+ \quad 37500i_1 = 275$$

$$i_1 = 6\text{mA} \quad i_2 = 8\text{mA}$$


$$\begin{aligned} P_{1kn2} &= (0,008 - 0,006)^2 \cdot 1000 = 0,004 \\ &= \underline{\underline{4\text{mW}}} \end{aligned}$$


c) I wouldn't because all I have to do is find the voltage of 10mA current source.

$$d) V_{10\text{mA}} + (0,01 - 0,006) \cdot 2500 + (0,01 - 0,007) \cdot 5000 = 0$$



$$\Rightarrow V_{10\text{mA}} = 20V$$
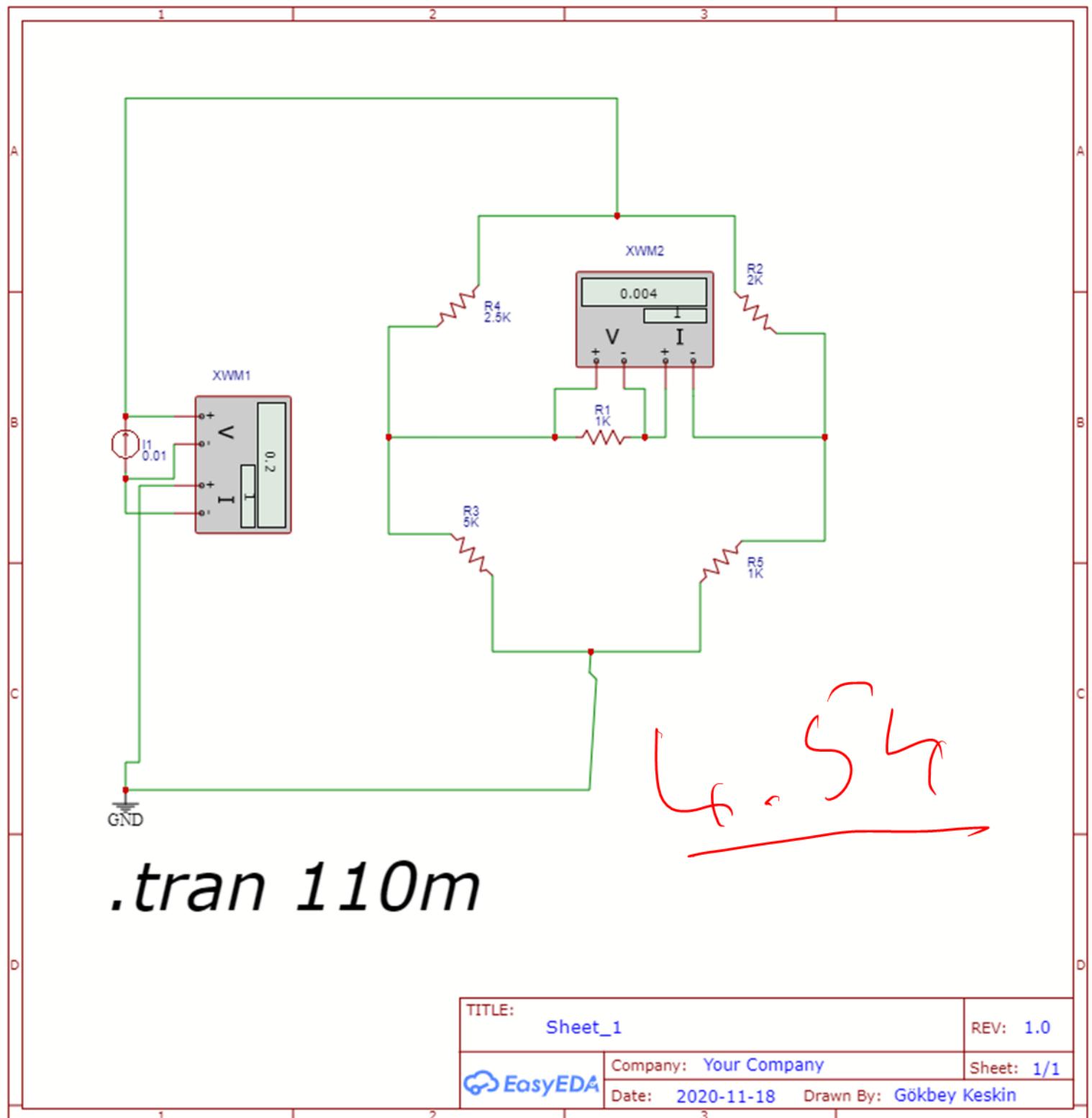
$$20 \cdot 0,01 = \underline{\underline{0,2\text{W}}}$$



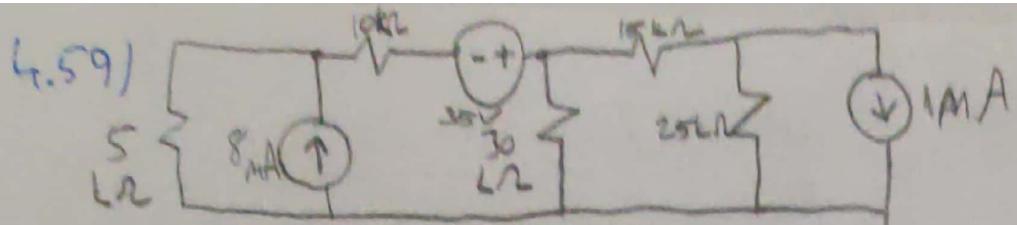


$$V = 0,008 \cdot 5000 = 40V$$

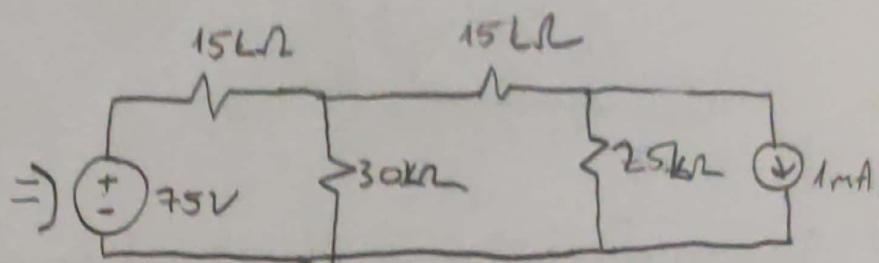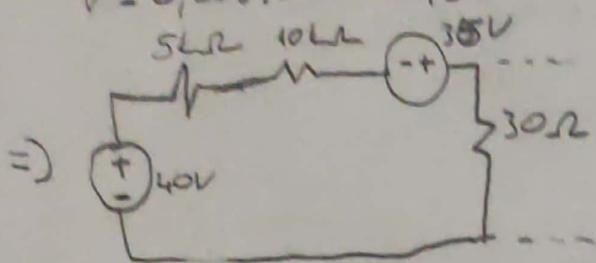

\Rightarrow

$$75 = 15000 \cdot i \Rightarrow i = 0,005A \quad | 15k\Omega || 30k\Omega = 10k\Omega$$

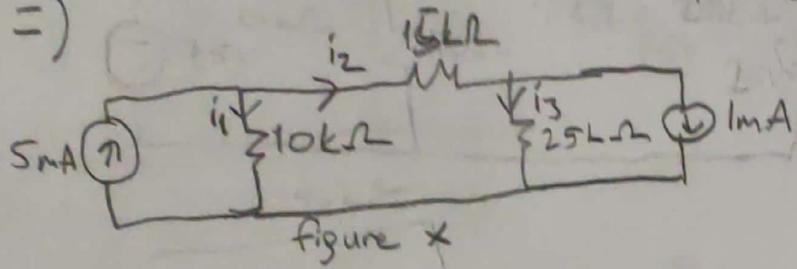

$$i_3 = \frac{0,005 \cdot 10}{50} + \left(-0,001 \cdot 25 \right) = 0,0005A$$

$$V_o = 0,0005 \cdot 25000 = \\ = 12,5V$$


=====

6) Mesh analysis for figure x


$$i \cdot 75 + (i-1) \cdot 25 + (i-5) \cdot 10 = 0,$$

$$50i = 75 \quad (1,5 - 1) \cdot 25 = \underline{\underline{12,5V}}$$
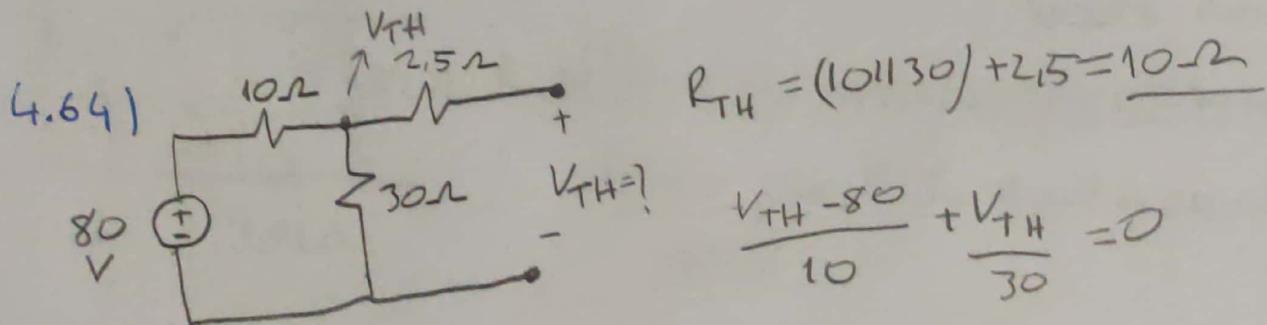
$$i = 1,5mA \quad (\text{mA}) \quad (k\Omega)$$


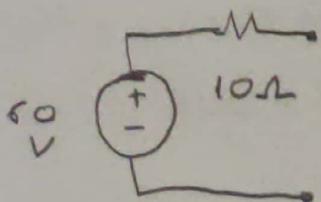
$$\frac{V_{TH} - 80}{10} + \frac{V_{TH}}{30} = 0$$




$$4V_{TH} = 240V$$

$$V_{TH} = \underline{\underline{60V}}$$


1

2

A

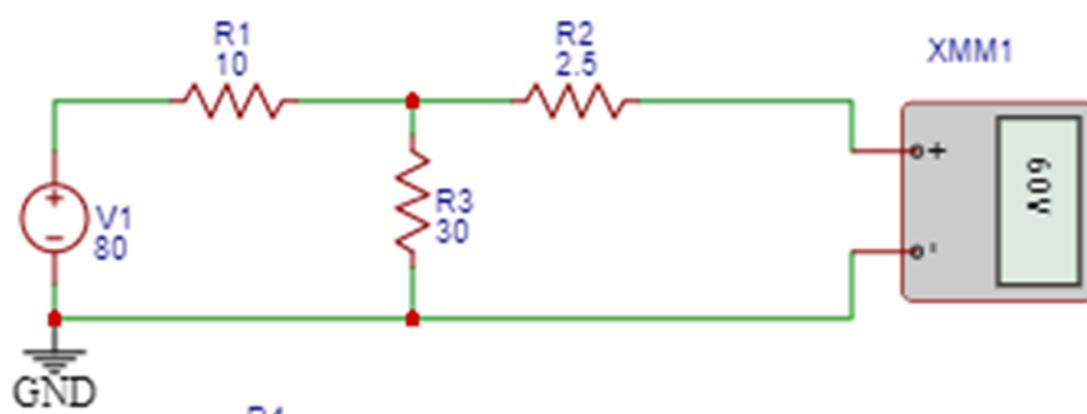

B

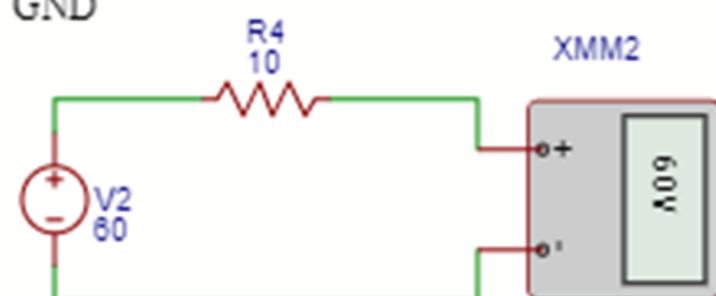


C

4, 64

.tran 10m

4.78)

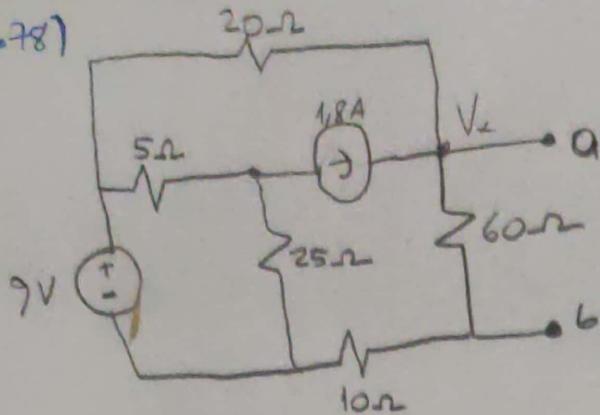


$$\frac{V_x}{20} - 1,8 + \frac{V_x - 9}{20} = 0$$


$$9V_x = 315$$

$$V_x = 35V$$


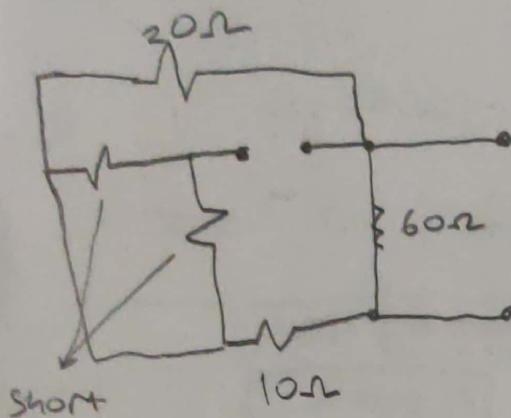
$$V_{TH} = \frac{35 \cdot 60}{70} = 30V$$


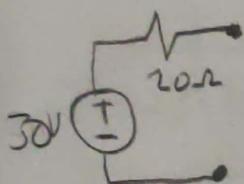
$$R_{TH} = [(20+10) \parallel 60] = 20\Omega$$



4.82)

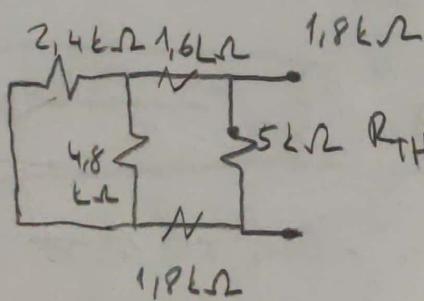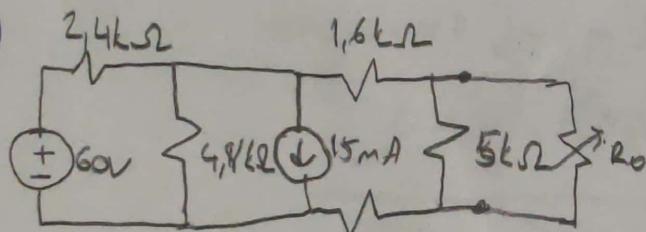

$$R_{TH} = ((2,4 \parallel 4,8) + 1,6) + 1,8 \parallel 15 = 2500\Omega$$

a) For max P Ro should be equal to R_{TH}

$$-60 + i_1 \cdot 2400 + (i_1 - i_2) 4800 = 0 \Rightarrow 7200i_1 - 4800i_2 = 60 \quad ①$$

$$(i_2 - i_1) \cdot 4800 + i_3 \cdot 1600 + i_3 \cdot 5000 + i_3 \cdot 1800 = 0 \Rightarrow -4800i_1 + 4800i_2 + 8400i_3 = 0 \quad ②$$


$$i_1 = 19,4mA, i_2 = 16,6mA, i_3 = 1,6mA$$

$$i_2 - i_1 = 0,015 \quad ③$$


$$V_{TH} = 5000 \cdot 0,016 = 8V$$


$$b) P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{64}{4 \cdot 2500} = 6,4mW$$
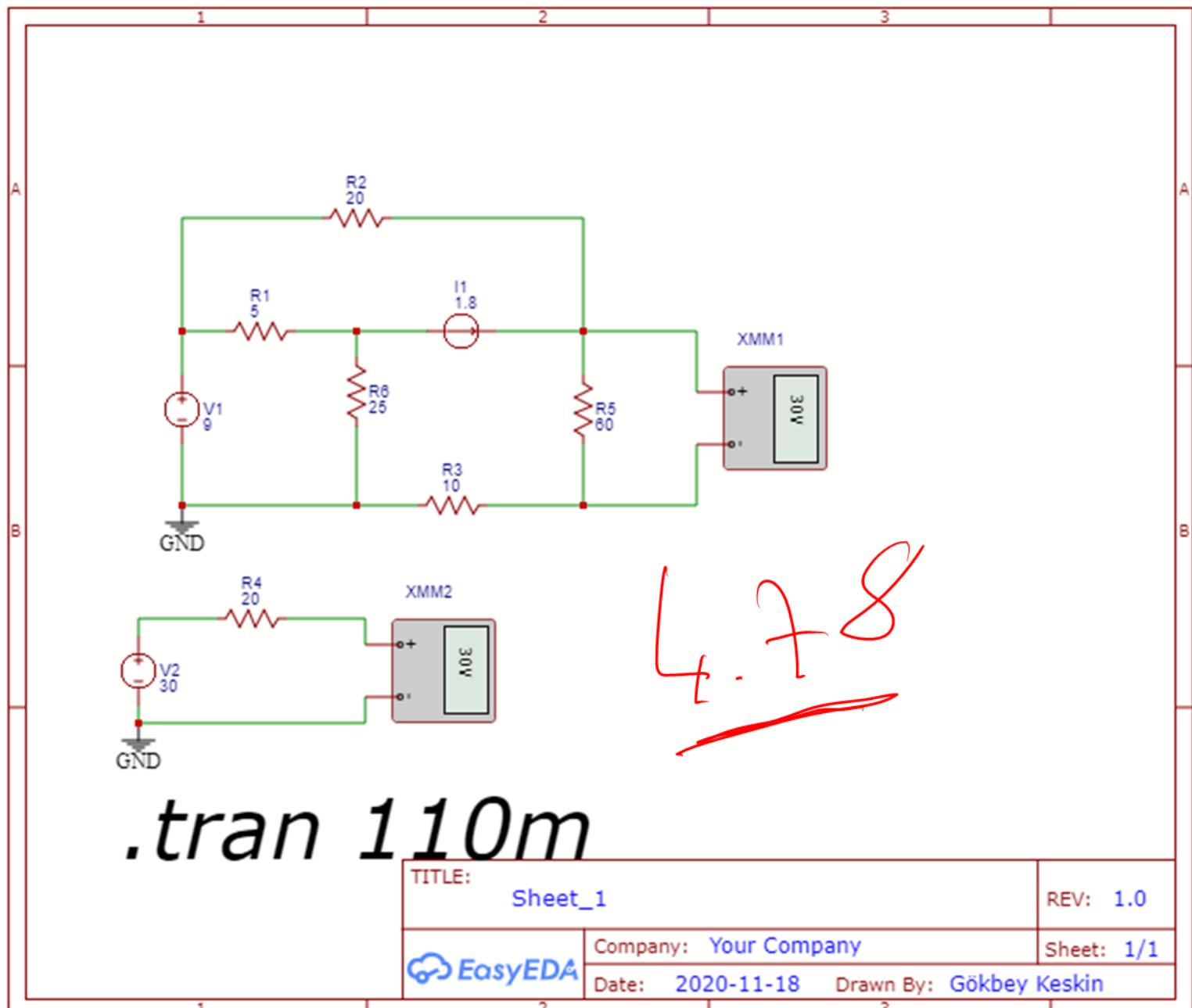
$$c) P_{2,7k} = \frac{V_{TH} \cdot R_0}{R_0 + R_{TH}} = \underline{6,391mW}$$



L-82

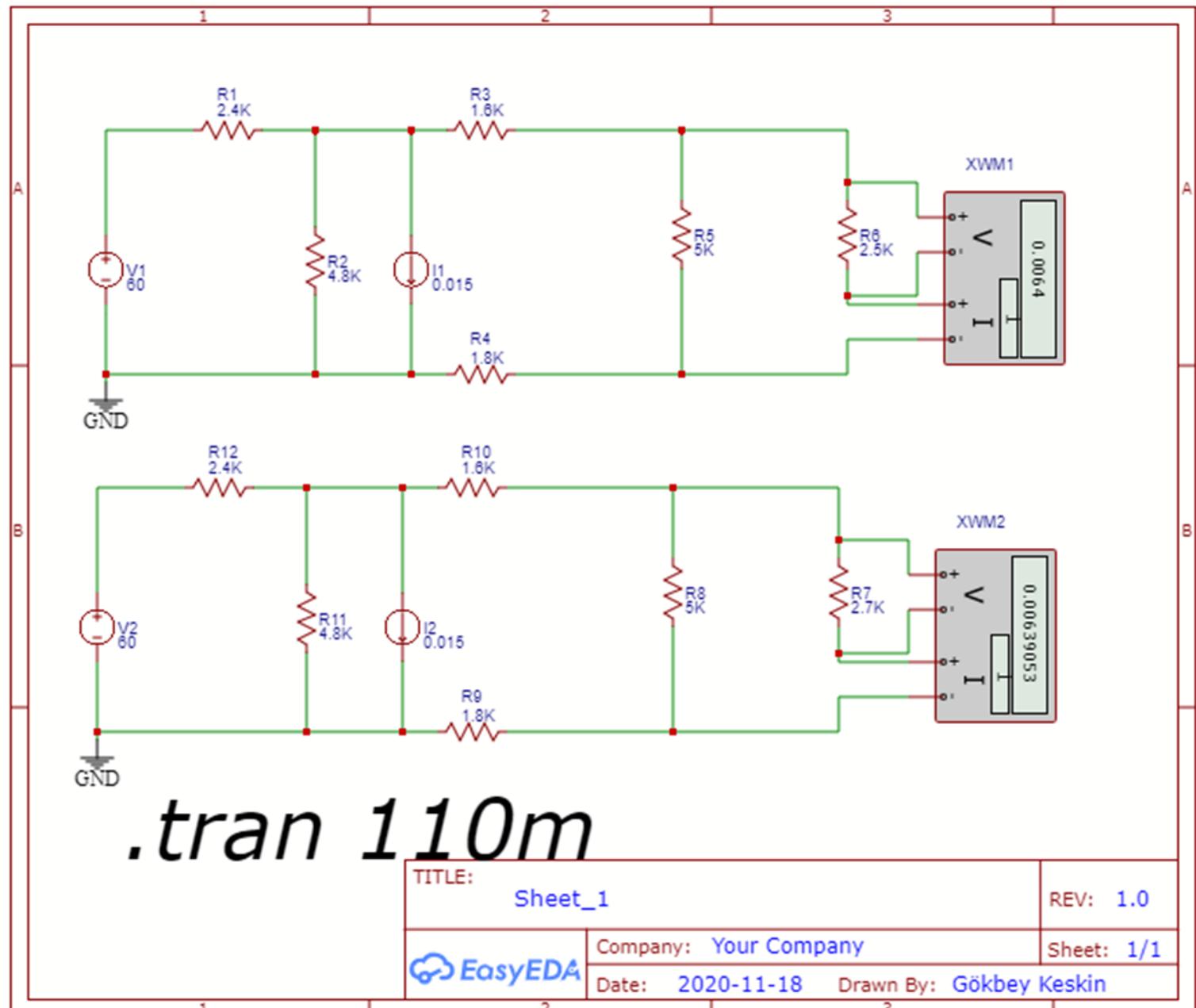

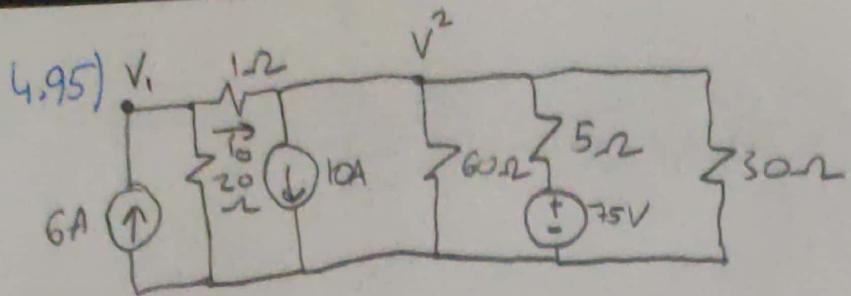

for only 10A source:

$$\frac{V_2' - V_1'}{1} + 10 + \frac{V_2'}{60} + \frac{V_2'}{5} + \frac{V_2'}{30} = 0 \Rightarrow 60V_2' - 60V_1' + 600 + V_1' + 12V_2' + 2V_2' = 0$$

$$75V_2' - 60V_1' = -600$$

$$\frac{V_1'}{20} + \frac{V_1' - V_2'}{1} = 0 \quad \longrightarrow \quad -20V_2' + 21V_1' = 0 \quad | \times 3,75$$

$$+ \quad \quad \quad$$

$$18,75V_1' = -600$$

$$\boxed{\begin{aligned} V_1' &= -32V \\ V_2' &= -33,6V \end{aligned}}$$

$$\boxed{i_o = \frac{-32 - (-33,6)}{1} = 1,6A}$$

for only 6A source:

$$-6 + \frac{V_1''}{20} + \frac{V_1'' - V_2''}{1} = 0 \quad \longrightarrow \quad 21V_1'' - 20V_2'' = 120 \quad | \times 3,75$$

$$\frac{V_2''}{30} + \frac{V_2''}{5} + \frac{V_2''}{60} + \frac{V_2'' - V_1''}{1} = 0 \Rightarrow -60V_1'' + 75V_2'' = 0$$

$$+ \quad \quad \quad$$

$$18,75V_1'' = 450V$$

$$\boxed{\begin{aligned} V_1'' &= 124V \\ V_2'' &= 19,2V \end{aligned}} \quad i_o = \frac{24 - 19,2}{1} = 4,8A$$

for only 75V source:

$$\frac{V_1'''}{20} + \frac{V_1''' - V_2'''}{1} = 0 \quad \longrightarrow \quad 21V_1''' - 20V_2''' = 0 \quad | \times 3,75$$

$$\frac{V_2'''}{30} + \frac{V_2''' - 75}{5} + \frac{V_2'''}{60} + \frac{V_2''' - V_1'''}{1} = 0 \Rightarrow 75V_2''' - 60V_1''' = 900$$

$$+ \quad \quad \quad$$

$$18,75V_1''' = 900$$

$$V_1''' = 48V$$

$$V_2''' = 50,4V$$

$$i_o''' = \frac{48 - 50,4}{1} = -2,4A$$

$$i_o = i_o' + i_o'' + i_o''' = 1,6 + 4,8 - 2,4 = \underline{\underline{4A}}$$

4-95

